

Josef Timmerberg, Prof. Dr.-Ing.

Electric Circuits

(10) 1.) DC Networks } 48 h
 (10) 2.) AC Network, 1 phase } 32 h
 (10) 4.) AC Network, 3 phase } 36 h
 X 5.) Induction motors

• Physical Values
 = quantity • unit
 ↓
 we can measure SI-System
 in SI-System: kg, m, s, A, K, rad.
 Basic Units →

• Multiplier + Submultiples of units

T	Tera	10^{12}
G		10^9
M		10^6
k	Kilo	10^3
m		10^{-3}
μ	micro	10^{-6}
n		10^{-9}
p	pico	10^{-12}

• Unit operator
 mass: m
 $[m] = \text{kg}$; $[t] = \text{s}$
 $[a] = ?$; $a = \frac{dv}{dt}$; $[a] = \left[\frac{dv}{dt} \right] = \frac{dv}{dt} = \frac{\Delta v}{\Delta t} =$

$[v] = ?$; $v = \frac{ds}{dt}$; $[v] = \left[\frac{ds}{dt} \right] = \left[\frac{\Delta s}{\Delta t} \right] = \frac{m}{s}$
 $[a] = \left[\frac{dv}{dt} \right] = \left[\frac{v}{t} \right] = \frac{m}{s \cdot s} = \frac{m}{s^2}$

~~$I = 4 \text{ esq}$~~
 $I = 4 \text{ mA}$
 $I = \frac{P}{t} = \frac{4 \text{ W}}{3 \text{ s}} = \frac{4}{3} \frac{\text{W}}{\text{s}}$

Units
 Basic elements in electrical eng.
 material consists of electrons, protons, neutrons
 $\frac{m_p}{m_e} \approx 10.000$

Charge electron → $q_e = -1.6 \cdot 10^{-19} \text{ As}$
 $= -1.6 \cdot 10^{-19} \text{ C}$
 $\rightarrow \text{DAC} = 1 \text{ As}$


Charge proton → $q_p = +1.6 \cdot 10^{-19} \text{ C}$
 ↳ elementary charge

$Q = n \cdot q_e$ charge in electrical eng.
 ↳ Integral


Charge is the basic of electrical eng.

→ Current definition:
 $I = \frac{dQ}{dt}$ spec: $I = \frac{Q}{t}$; $[Q = It] = \text{As} = \text{C}$

Source: voltage source, current I .

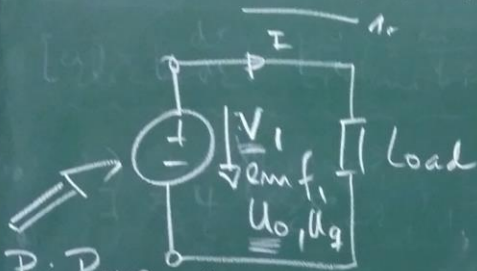

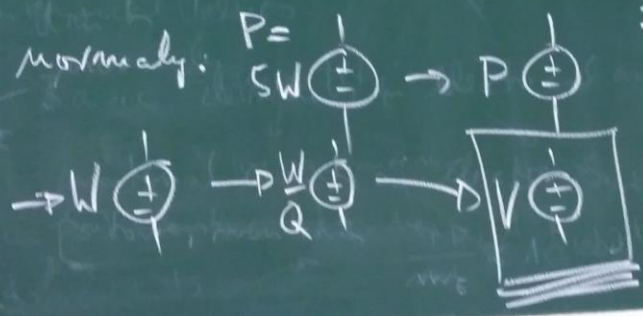
P : Power
 W : Work } energy, work \neq electrical
 P, W : thermal, mechanical, optical



Power
 \uparrow
 $[P] = W$
 $[W] =$

$$\left[\frac{W}{Q} \right] = \frac{J}{C} = \frac{W \cdot s}{A \cdot s} = \frac{VA}{A} = V$$
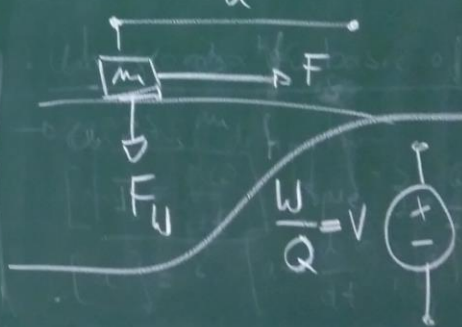
$$[W = F \cdot s = F \cdot d] = N \cdot m = J = W \cdot s$$




V : Potential Difference

Very important

$$1 \text{Ws} = 1J = 1Nm$$

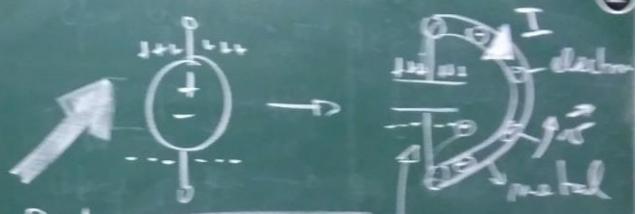Example 2.2: 300mC
 $V = 100 \text{V}$
 $W = Q \cdot V = 300 \text{mC} \cdot 100 \text{V}$
 $= \frac{300 \cdot A \cdot s \cdot 100 \text{V}}{1000}$
 $= 30 \text{VAs} = 30 \text{Ws}$



P, W


$$W = \int P dt$$

$$P = \frac{dW}{dt}$$

$$\vec{v}_e \Rightarrow -I$$

Def. Direction of current is opposite dir. of electrons


Symbol of voltage sources:

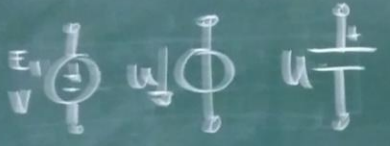


practical source battery

↳ ideal voltage source
(in opposite to technical volt. s.)

characterization of a volt. source:

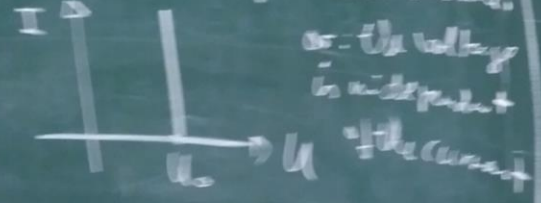

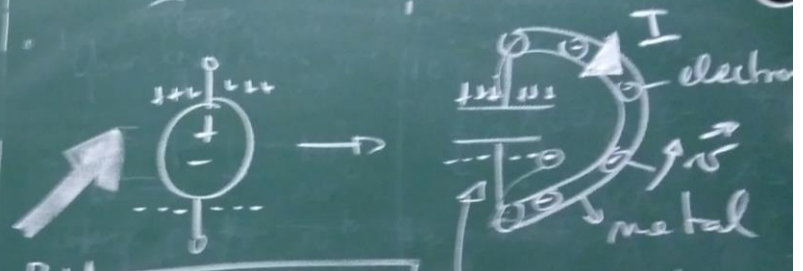or: the voltage is independent of the current



$$P, U \quad U = \int P dt$$


$$P = \frac{dW}{dt}$$

$$\vec{v}_0 \Rightarrow -I \quad \equiv$$

high density of neg. ions

Def. Direction of current: opposite dir. of electrons


Symbol of voltage sources:

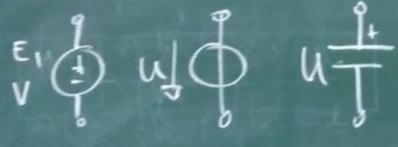

practical source battery


↳ ideal voltage source
(in opposite to technical volt. s.)

characterization of a volt. source:

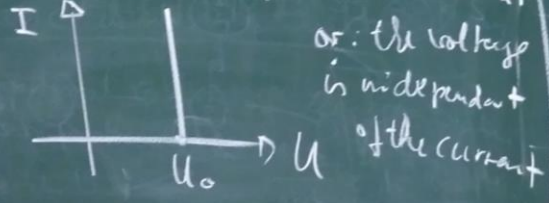


or: the voltage is independent of the current

Current source, ideal

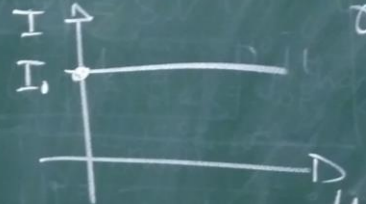

or: the current is independent of the voltage


Example

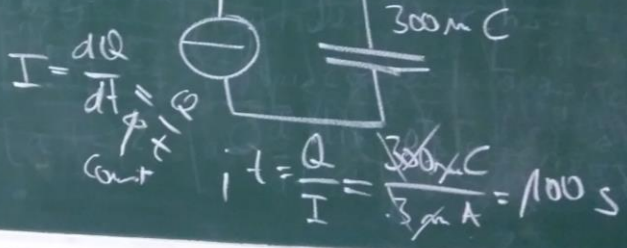

$$I = \frac{dQ}{dt} = \frac{Q}{t} \quad \text{Cont.}$$

$$t = \frac{Q}{I} = \frac{300 \mu C}{3 \mu A} = 100 s$$

Olaus law

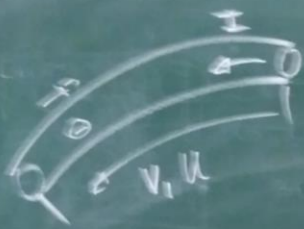

Obs: $V = U \sim I \rightarrow \text{prop.}$

$\begin{cases} F \sim a \Rightarrow \\ \text{Eq. } F = ma \end{cases}$

$$V = U = RI$$

\rightarrow in experiment




complicated | simple

the box $\begin{matrix} | \\ R \\ | \end{matrix}$ stands for the wire, a general wire. We call it resistor R


Obs: $R = \frac{U}{I} = \text{const}$
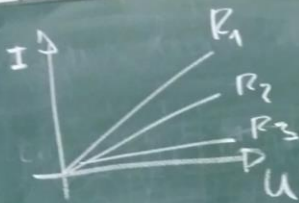
$$[R] = \left[\frac{V}{I} \right] = \frac{V}{A} = \Omega; \text{ ex: } R = 7\Omega$$





all R_s are linear

$$R_1 < R_2 < R_3$$

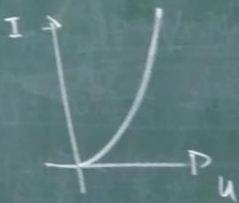

R is not linear

Symbol of R

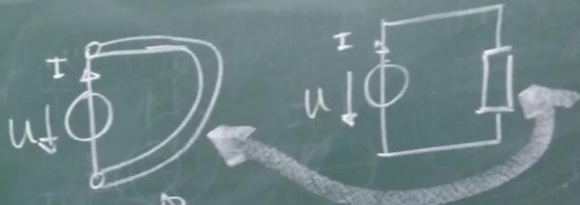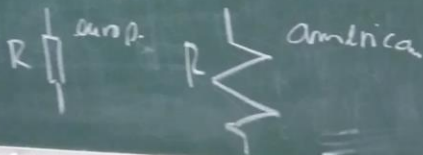

complicated | simple

the box $\begin{matrix} | \\ R \\ | \end{matrix}$ stands for the wire, a general wire. We call it resistor R


Obs: $R = \frac{U}{I} = \text{const}$

$$[R] = \left[\frac{V}{I} \right] = \frac{V}{A} = \Omega; \text{ ex: } R = 7\Omega$$

- law of Ohm see above
- laws of Kirchhoff


- 1.) Kirchhoff 1
- 2.) Kirchhoff 2

$$\sum_{k=1}^n I_{k\text{out}} = 0$$

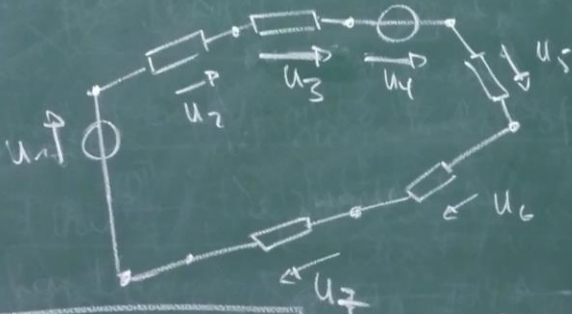

$$\sum_{k=1}^n U_k = 0$$


change the direction

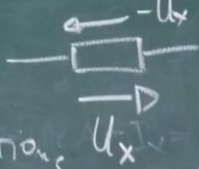

with the same directions of all voltages

Combinations of R

in series

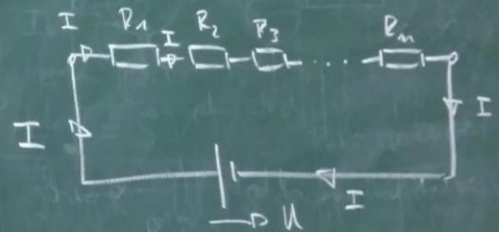


in a circuit without a node can flow only one current

→ stop

- law of Ohm see above
- laws of Kirchhoff


- 1.) Kirchhoff 1
- 2.) Kirchhoff 2

$$\sum_{k=1}^n I_{k\text{out}} = 0$$

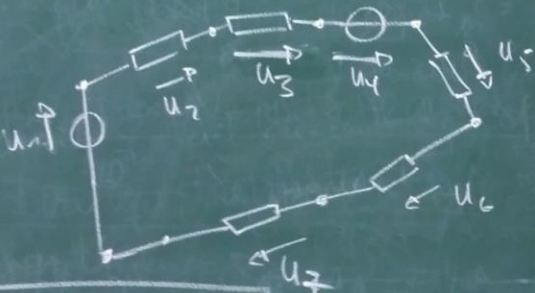

$$\sum_{k=1}^n U_k = 0$$


change the direction

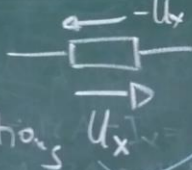

with the same directions of all voltages

Combinations of R

in series

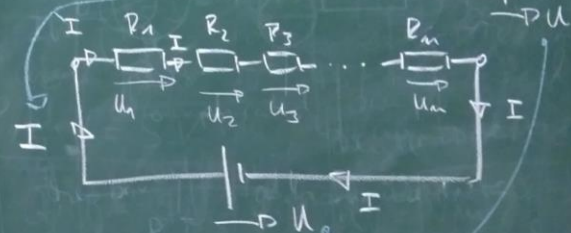

in a circuit without a node can flow only one current

→ stop

$$U_1 + U_2 + U_3 + \dots + U_n - U = 0$$


$$I R_1 + I R_2 + I R_3 + \dots + I R_n = U$$

$$(R_1 + R_2 + R_3 + \dots + R_n) I = U$$

$$R_1 + R_2 + R_3 + \dots + R_n = \frac{U}{I} = R; \quad R = \sum_{k=1}^n R_k$$

$$R = \sum_{k=1}^n R_k$$

example:

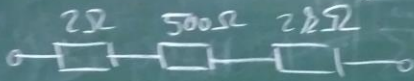


What is the substitution for

$$R = 2\Omega + 500\Omega + 22\Omega$$

$$= \underline{\underline{252\Omega}}$$

Combinations of R

in series

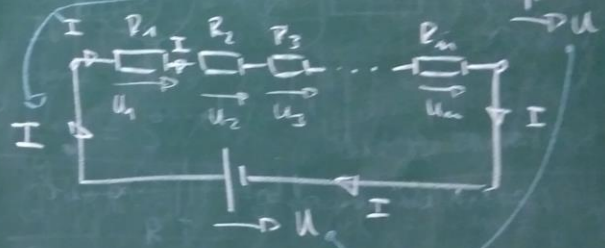

in a circuit without a node can flow only one current

→ stop

$$U_1 + U_2 + U_3 + \dots + U_n - U = 0$$

$$I R_1 + I R_2 + I R_3 + \dots + I R_n = U$$

$$(R_1 + R_2 + R_3 + \dots + R_n) I = U$$

$$R_1 + R_2 + R_3 + \dots + R_n = \frac{U}{I} = R$$


$$R = \sum_{k=1}^n R_k$$

Ohm's law

kindest I, R

Resistor in series

Resistor parallel

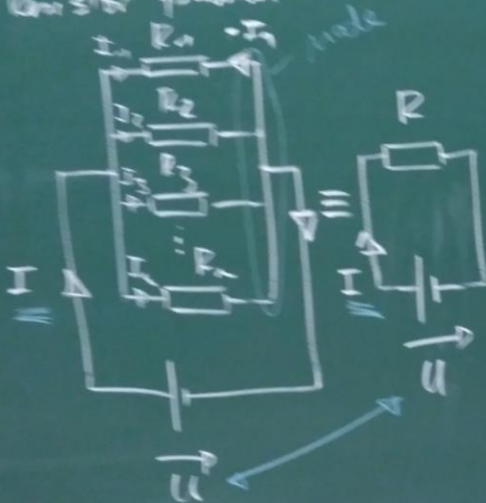

$$\sum_{k=1}^n I_k = I_1 + I_2 + I_3 + \dots + I_n - I = 0$$

equal to: $-I_1 - I_2 - I_3 - \dots - I_n + I = 0$

$$\frac{U}{R_1} + \frac{U}{R_2} + \frac{U}{R_3} + \dots + \frac{U}{R_n} - \frac{U}{R} = 0$$

$$U = R \cdot I, I = \frac{U}{R}$$

$$\frac{1}{R} = \sum_{k=1}^n \frac{1}{R_k}$$


$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} = \frac{1}{R}$$

spec. case $n=2$:

$$\frac{1}{R} = \frac{1}{R_1} + \frac{1}{R_2} \quad R = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2}\right)} = \frac{R_1 R_2}{R_1 + R_2}$$

$$R = \frac{R_1 R_2}{\frac{R_1 R_2}{R_1} + \frac{R_1 R_2}{R_2}} = \frac{R_1 R_2}{R_1 + R_2} = R$$

ex. ple:

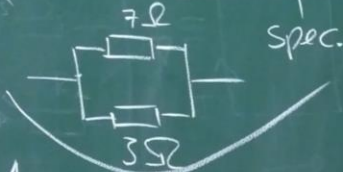

$$\frac{1}{R} = \frac{1}{7\Omega} + \frac{1}{3\Omega} = \dots \text{dif.}$$

$$R = \frac{7\Omega \cdot 3\Omega}{10\Omega} = 2.1\Omega$$

$$\sum_{k=1}^n I_k = I_1 + I_2 + I_3 + \dots + I_n - I = 0$$

equal to: $-I_1 - I_2 - I_3 \dots - I_n + I = 0$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} - \frac{1}{R} = 0$$


$$V = R \cdot I, \quad I = \frac{V}{R}$$

$$\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n} = \frac{1}{R}$$

$$\frac{1}{R} = \sum_{k=1}^n \frac{1}{R_k}$$

general

Resistivity of a straight wire

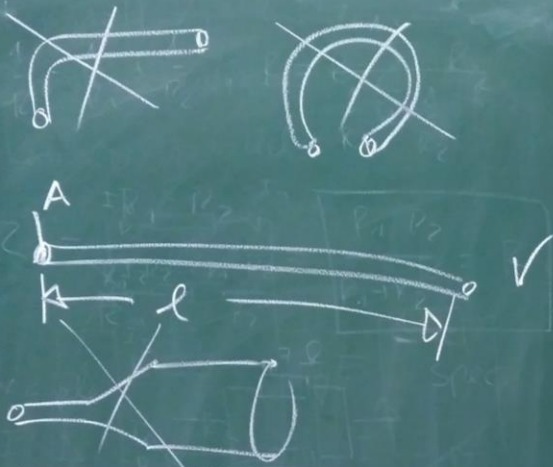

$$R = s \frac{l}{A} = \frac{1}{\sigma} \frac{l}{A}$$

σ = Conductivity in $\frac{m}{\Omega}$
 s = specific resistance in $\frac{\Omega}{m}$

$$\sigma = \frac{1}{s} \quad G = \frac{1}{R} \quad \text{conductivity}$$

$$[R] = \Omega = \frac{V}{A}$$

$$[G] = \frac{1}{\Omega} = \frac{A}{V} = S$$



Example: A wire with the length of 32m and the area $A = 3 \text{ cm}^2$ of Cu: has resist R ?

$$R = \frac{\rho \cdot l}{A} = \frac{1.7 \cdot 10^{-8} \Omega \cdot \text{m} \cdot 32 \text{ m}}{3 \cdot 10^{-6} \text{ m}^2} = 1.81 \cdot 10^{-1} \Omega$$

$$\rho_{\text{Cu}} = 1.7 \cdot 10^{-8} \frac{\Omega}{\text{m}} \text{ page 16}$$

$$= \frac{1.7 \cdot 10^{-8} \cdot 32}{3 \cdot 10^{-6}} = \frac{1}{6} \Omega$$

G = Conductivity in $\frac{\text{m}}{\Omega}$
 ρ = specific resistance in $\frac{\Omega}{\text{m}}$



$$\sigma = \frac{1}{\rho} \quad G = \frac{1}{R} \text{ - conductivity}$$

$$[R] = \Omega = \frac{V}{A}$$

$$[G] = \frac{1}{\Omega} = \frac{A}{V} = S$$




Real sources
 - real voltage source

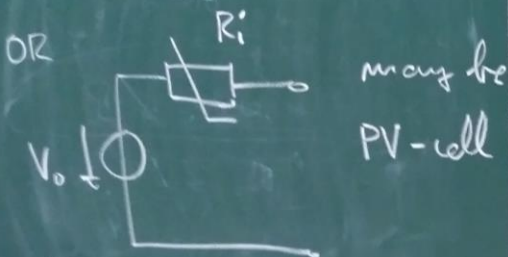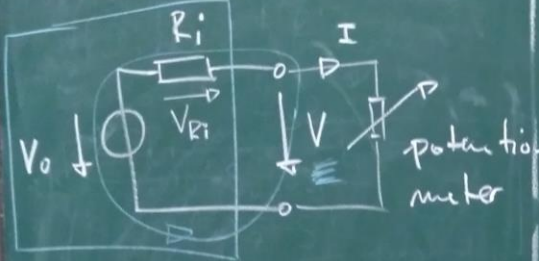

R_i = internal resistor

non linear resistor

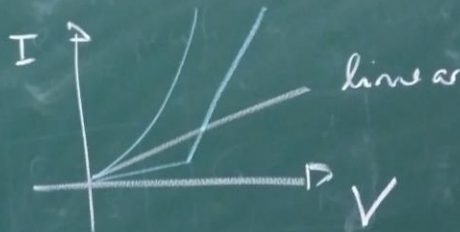





We take R_i as linear (first)

→ we want to calculate $V(R_i, V_0)$

$$V_{R_i} = R_i \cdot I \quad \sum V_k = V_{R_i} + V - V_0 = 0$$

$$V = V_0 - V_{R_i} = V_0 - R_i \cdot I$$

$$\boxed{V = V_0 - R_i \cdot I}$$

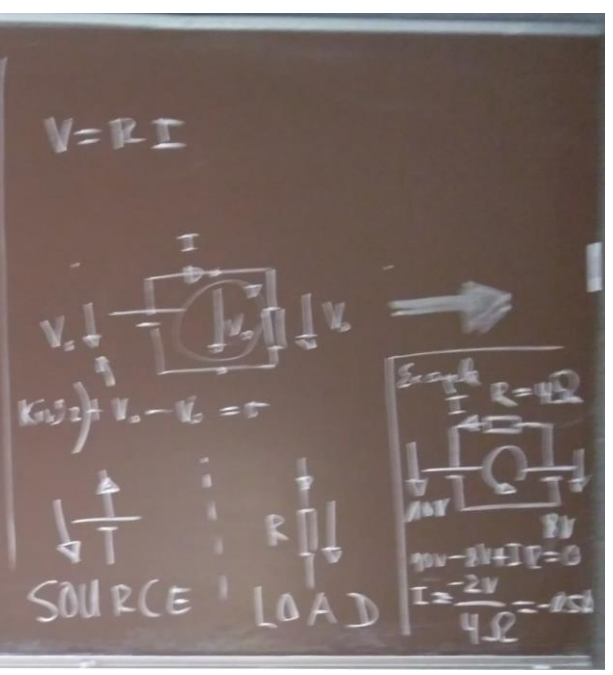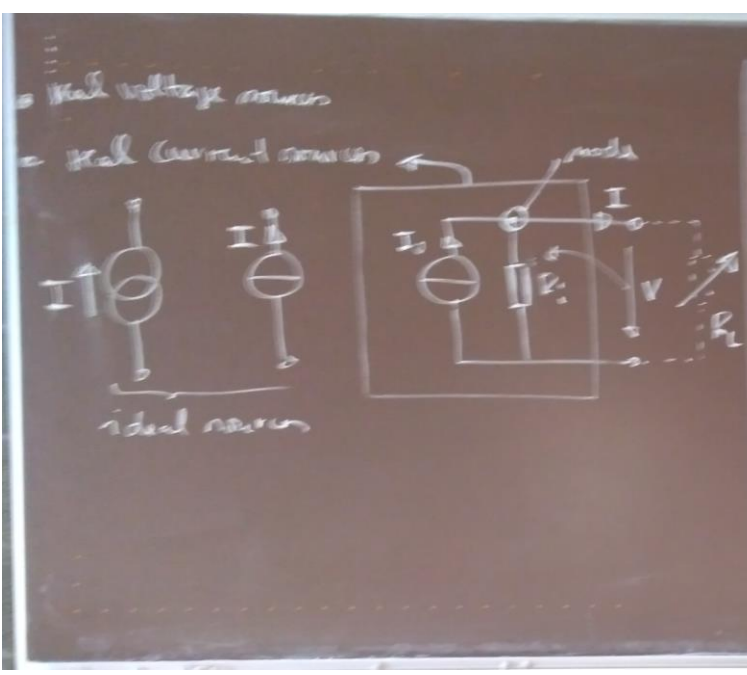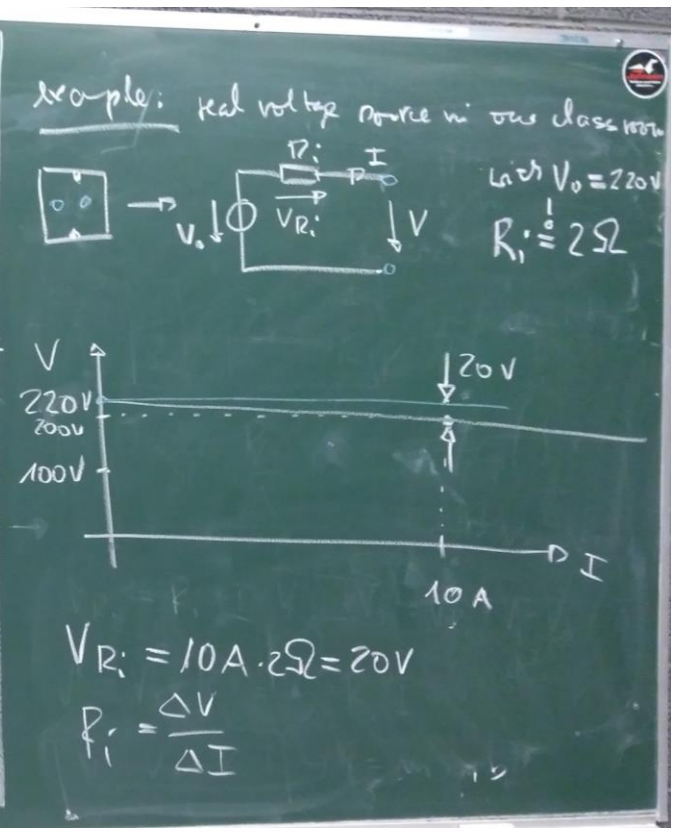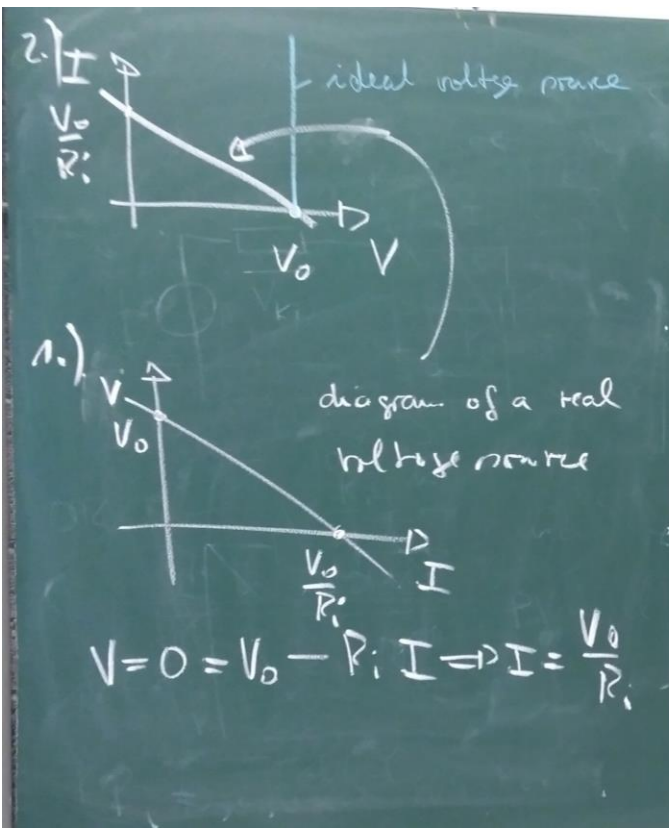

Real voltage sources

Real current sources

ideal sources

mode

$V = RI$

$Kirchhoff) V_0 - V_0 = 0$

Example $R = 4\Omega$

$10V - 8V + IR = 0$

$I = \frac{-2V}{4\Omega} = -0.5A$

SOURCE

LOAD

Real voltage sources

Real current sources

ideal sources

mode

$\sum I = I_0 + (-I) + (-I_{R_i}) = 0$

$I_0 - I - I_{R_i} = I_0 - I - \frac{V}{R_i} = 0$

$V = (I_0 - I)R_i = I_0 R_i - R_i I$

ideal current source

real curr. source

$V_0 = I_0 R_i$


Real voltage source

• Real voltage sources


• Real current sources

You can transform a real voltage source into a real current source, if $V_0 = I_0 \cdot R_i$


OR

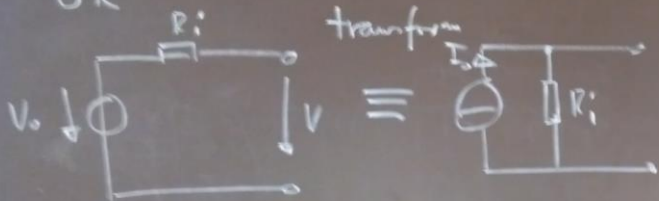

Example:

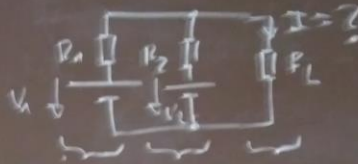
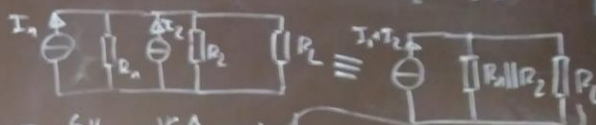
$$\begin{aligned} R_1 &= 2\Omega \\ R_2 &= 2\Omega \\ R_L &= 4\Omega \\ V_1 &= 6V \\ V_2 &= 5V \end{aligned}$$




$$I_1 = \frac{6V}{2\Omega} = 3 \frac{V}{\Omega} = 3A$$

$$I_2 = 2.5A$$

$$I_1 + I_2 = I_3 = 5.5A$$
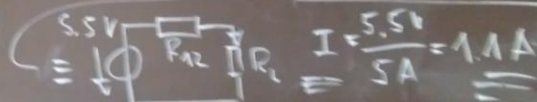
$$R_1 \parallel R_2 = R_{12} = \frac{R_1 \cdot R_2}{R_1 + R_2} = 1\Omega$$




$$I = \frac{5.5V}{5\Omega} = 1.1A$$

• Real current source

• abstract circuit analysis

definition:

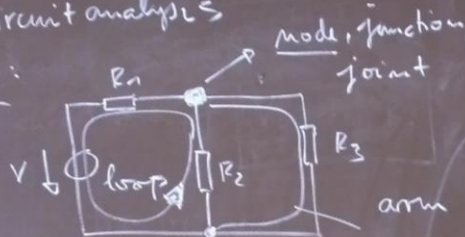


loop: closed, has a (free) direction

arm: consists of one resistor and a voltage source and ends in two nodes

= closed path over arms and nodes.

independent equations:

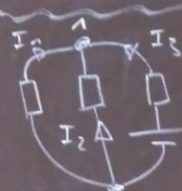

goal of network calcul.

if R_k and V_i are given, you have to calculate the currents I_1, I_2, I_3

$$\textcircled{1} I_1 + I_2 + I_3 = 0$$

$$\textcircled{2} -I_1 - I_2 - I_3 = 0$$

$$-I_1 + I_2 + I_3 = 0$$

$$\text{Similar} \quad \underline{I} = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$$

- Ideal current source
- abstract circuit analysis

definition:

mode, junction, joint

loop: closed, has a (pre)direction

arm: consists of one resistor and a voltage source and ends in two modes

= closed path over arms and modes.

independent equations:

goal of network calculation: if R_k and V_i are given you have to calculate the currents I_1, I_2, I_3

$\textcircled{1} : I_1 + I_2 + I_3 = 0$
 $\textcircled{2} : -I_1 - I_2 - I_3 = 0$
 $\textcircled{3} : I_1 + I_2 + I_3 = 0$

OR $\underline{I} = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$

- Ideal current source
- abstract circuit analysis

definition:

mode, junction, joint

loop: closed, has a (pre)direction

arm: consists of one resistor and a voltage source and ends in two modes

= closed path over arms and modes.

independent equations:

goal of network calculation: if R_k and V_i are given you have to calculate the currents I_1, I_2, I_3

$\textcircled{1} : I_1 + I_2 + I_3 = 0$
 $\textcircled{2} : -I_1 - I_2 - I_3 = 0$
 $\textcircled{3} : I_1 + I_2 + I_3 = 0$

OR $\underline{I} = \begin{pmatrix} I_1 \\ I_2 \\ I_3 \end{pmatrix}$

Similar

→ if we have a network with n modes, it produces only $n-1$ equations

Voltage is important

$$\boxed{1 \text{ Ws} = 1 \text{ J} = 1 \text{ Nm}}$$


Example 2.2: 300 mC

$$V = 100 \text{ V}$$

$$W = Q \cdot V = 300 \text{ mC} \cdot 100 \text{ V}$$

$$= \frac{300 \cdot \text{As} \cdot 100 \text{ V}}{1000}$$

$$= 30 \text{ VAs} = 30 \text{ Ws}$$

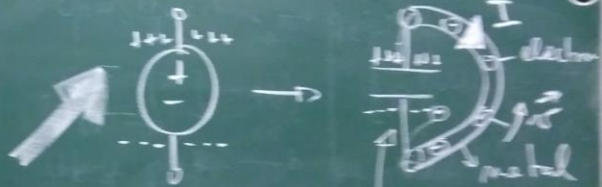

$$P, W$$


$$W = \int P dt$$

$$P = \frac{dW}{dt}$$

$$\vec{v}_e \Rightarrow -I +$$

high density of neg. chg.
Def. Direction of current is opposite dir. of electrons



Symbol of voltage sources:

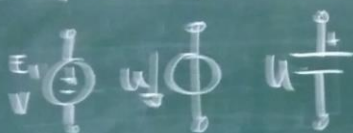

independent source battery

↳ ideal voltage source
(is opposite to ideal volt. s.)

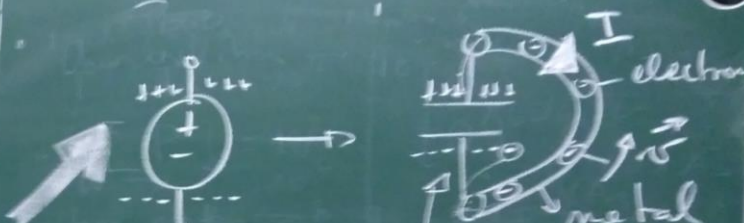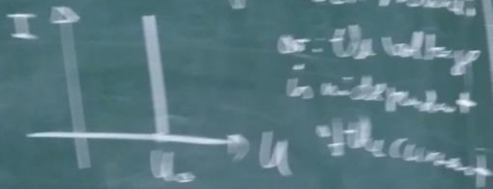direction of a volt. source
or: the voltage is independent
of the current



$$P, W$$


$$W = \int P dt$$

$$P = \frac{dW}{dt}$$

$$\vec{v}_e \Rightarrow -I +$$


high density of neg. chg.
Def. Direction of current is opposite dir. of electrons

Symbol of voltage sources:

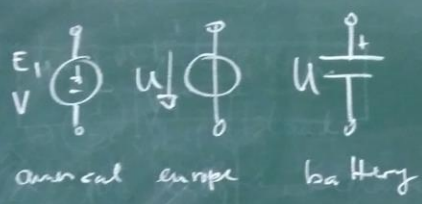



↪ ideal voltage source
(in opposite to terminal volt. s.)

Characterization of a volt. source:

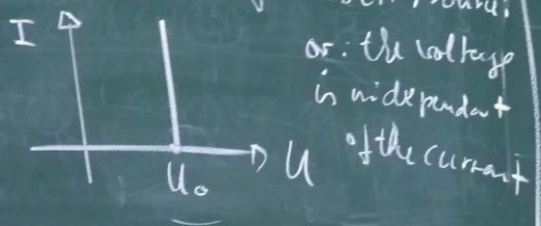


or: the voltage is independent of the current

Current source, ideal

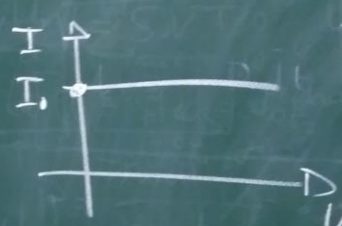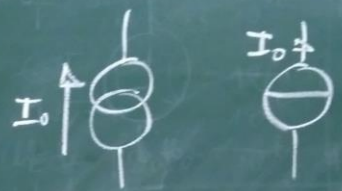

or: the current is independent of the voltage

Example

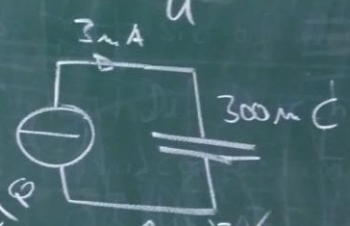

$$I = \frac{dQ}{dt} = \frac{Q}{t}$$

$$t = \frac{Q}{I} = \frac{300 \mu\text{C}}{3 \mu\text{A}} = 100 \text{ s}$$