

# Electric Circuits, Review ①

25.03.19

• Continue with photo 153458.p  
• jpg  
⋮

• What we need:

▷ Kirchhoff law 1:  $\sum_{k=1}^n I_k = 0$


▷ Kirchhoff law 2:  $\sum_{k=1}^n U_k = 0$

▷ Ohm's law  $U = R \cdot I$

② ▷ if our network consist of  $n$  nodes, ~~we~~ we get  $n-1$  equation of this from Kirchhoff 1

▷ the rest of the equations we get from Kirchhoff 2. Therefore we need a tree.

▷ We learn on an example

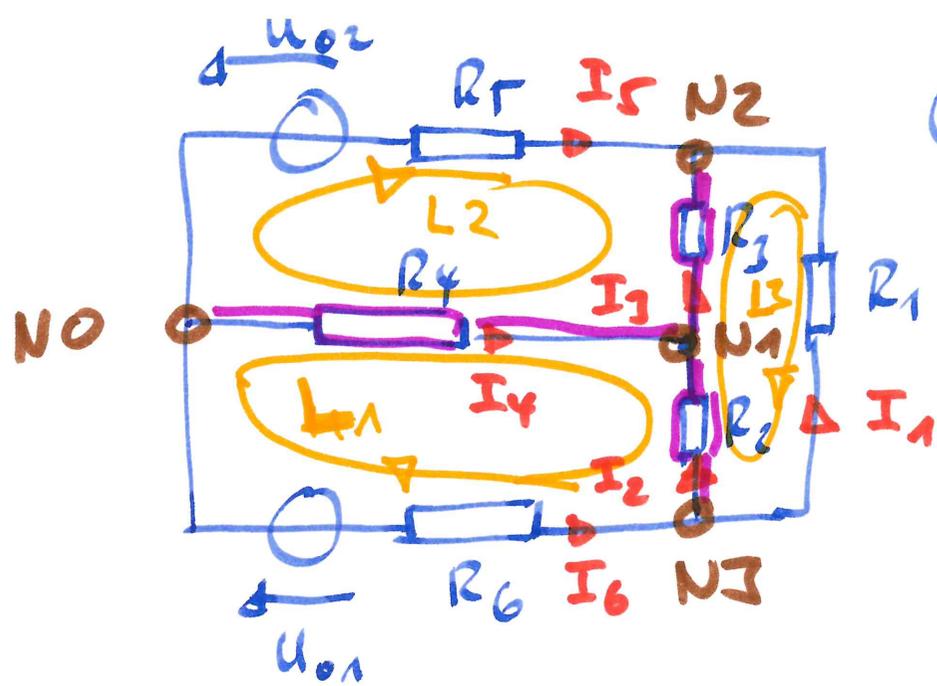

③

④

branch has a current |  
 If we have  $z$  branches,  
 we need  $z$  currents  $\Rightarrow$   
 We get an  $z \times z$  equation  
 system.

- In reality: Sources are given and cables, loads are given. We take this also:

$$U_{0i}, R$$

Goal of the calculation:

$\Rightarrow$  To calculate the currents in the branches. (Each

- 1.) We number the branches from  $1 \dots z$
- 2.) In the branches we define the currents from  $I_1 \dots I_z$
- 3.) We number the nodes from  $N_0 \dots N_n - 1$  and do not take  $N_0$
- 4.) We sketch a tree in to

- number of equations (5)

4 nodes gives 3 equations

6 loop " 6 " "  
9 " !

We need 6 currents =

6 equations  $\Rightarrow$

3 equations  $\rightarrow$  from nodes

3 " " loops  
6 " "

We get this 3 independent equations, ~~not~~ with the tree

(6)

- tree is a construction with all nodes but without any loop  $\Rightarrow$  branches of the tree is node number

$-1$  !  $(n-1) \equiv$  the number of equations we get from Kirchhoff 1.

- not-tree-branch =  $z - (n-1)$   
 $= 3$

We build loop with <sup>only</sup> one not-tree-branch. L1, L2, L3

So we get 3 independent equations.

$$N1: +I_2 + I_4 - I_3 = 0$$

$$N2: I_1 + I_3 + I_5 = 0$$

$$N3: +I_6 - I_2 - I_1 = 0$$

$$L1: R_4 I_4 - R_2 I_2 - R_6 I_6 + U_{01} = 0$$

$$L2: R_5 I_5 - R_3 I_3 - R_4 I_4 - U_{02} = 0$$

$$L3: R_3 I_3 - R_1 I_1 + R_2 I_2 = 0$$

$$\begin{pmatrix} 0 & 1 & -1 & 1 & 0 & 0 \\ 1 & 0 & 1 & 0 & 1 & 0 \\ -1 & -1 & 0 & 0 & 0 & 1 \\ 0 & -R_2 & 0 & R_4 & 0 & -R_6 \\ 0 & 0 & -R_3 & -R_4 & R_5 & 0 \\ -R_1 & R_2 & R_3 & 0 & 0 & 0 \end{pmatrix} \begin{pmatrix} I_1 \\ I_2 \\ I_3 \\ I_4 \\ I_5 \\ I_6 \end{pmatrix} = \begin{pmatrix} 0 \\ 0 \\ 0 \\ -U_{01} \\ U_{02} \\ 0 \end{pmatrix}$$

⑦

⑧

Example with values

$$R_i = i \cdot 10 \Omega; U_{0i} = i \cdot 100V$$

Equation system

$$\underline{A} \cdot \underline{x} = \underline{b}$$

We want to calculate

$$\underline{x} = \begin{pmatrix} x_1 \\ x_2 \\ \vdots \end{pmatrix} = \begin{pmatrix} b_1 \\ b_2 \\ \vdots \end{pmatrix}$$

$$\underline{A}^{-1} \cdot \underline{A} \cdot \underline{x} = \underline{A}^{-1} \underline{b}$$

$$\underline{E} = \underline{1}$$

$$\underline{1} \cdot \underline{x} = \underline{x} = \underline{A}^{-1} \underline{b}$$

! Do not use the **OK** button,


use **Shift** + **Strg** + **Enter**!

# Electric Circuits, Review

25.3.19 (2)

## Energy, Power, Losses on transmission lines

Our standard circuit

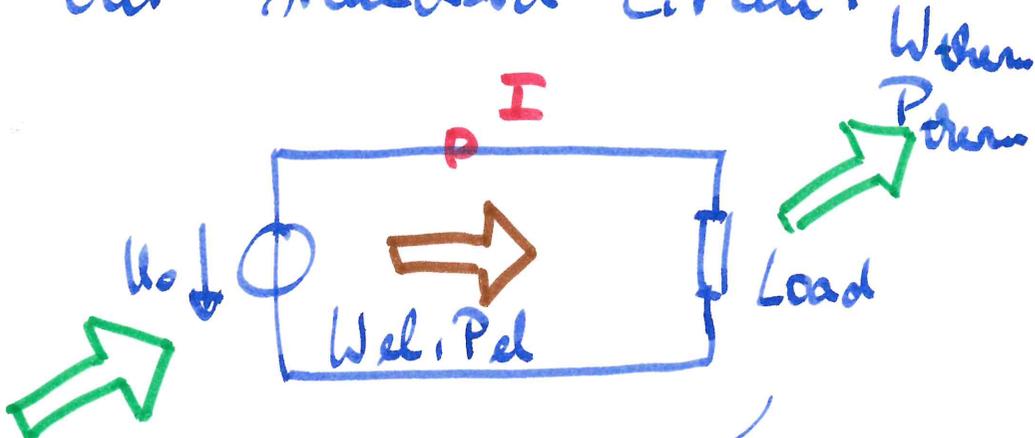

Energy transmission

$W$ : Work;  $P$ : Power

①


②

$$P = U \cdot I \rightarrow \text{Power in W}$$

$$W = \int P dt \rightarrow \text{Work in Ws}$$


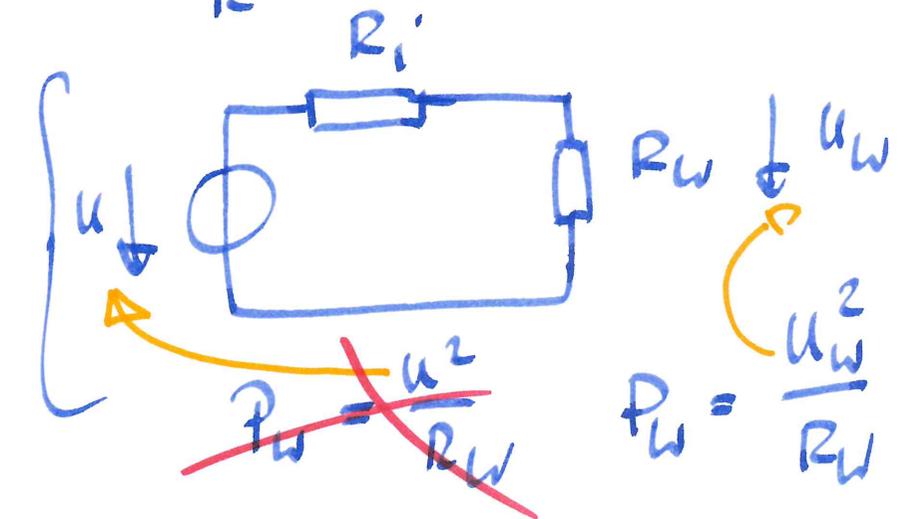
$$P = U I = I^2 \cdot R = \frac{U^2}{R}$$



3 formats of power!


$$[P] = W = V \cdot A$$

③

From Power to Work = Energy:

$$W = \int_0^t P(t) dt \quad \text{in Ws}$$

Electric circuits with transmission line

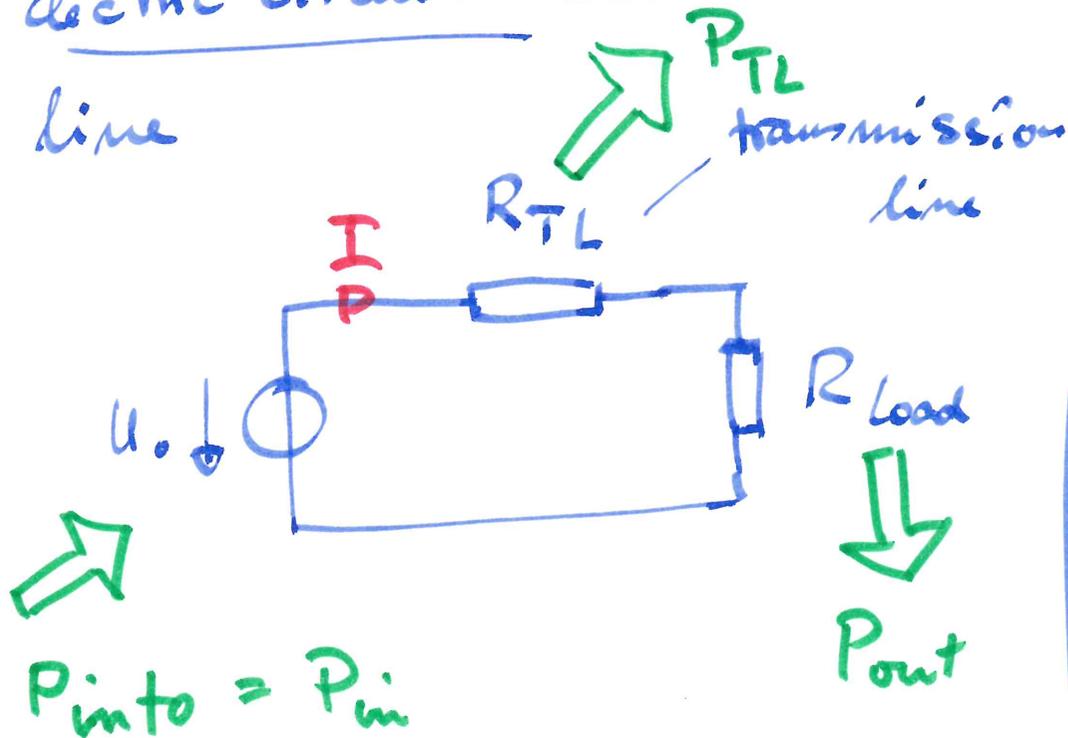

④

$$\eta_P = \frac{P_{out}}{P_{in}} = \frac{P_{out}}{P_{TL} + P_{out}} = < 1$$

efficiency factor

Similar:

$$\eta_W = \frac{W_{out}}{W_{in}} \leq 1$$

↳ Energy