

EC, 24.4.19

①

Alternating voltage, alternating current

∴ see last lesson

$$u(t) = \hat{u} \cdot \sin(\omega t + \varphi_u)$$

$$= \text{Im} \left\{ \hat{u} e^{j(\omega t + \varphi_u)} \right\}$$

Go on

For $i(t) = \hat{i} \cdot \sin(\omega t + \varphi_i)$

$$= \text{Im} \left\{ \hat{i} e^{j(\omega t + \varphi_i)} \right\}$$

part

③

it's jode-hs. de

②


$$e^{j\varphi} = \cos(\varphi) + j \sin(\varphi)$$

substitution:

$$\hat{u} = U_{eff} \cdot \sqrt{2} = U \cdot \sqrt{2}$$

$$\hat{i} = I_{eff} \cdot \sqrt{2} = I \cdot \sqrt{2}$$

• R to alternating voltage source

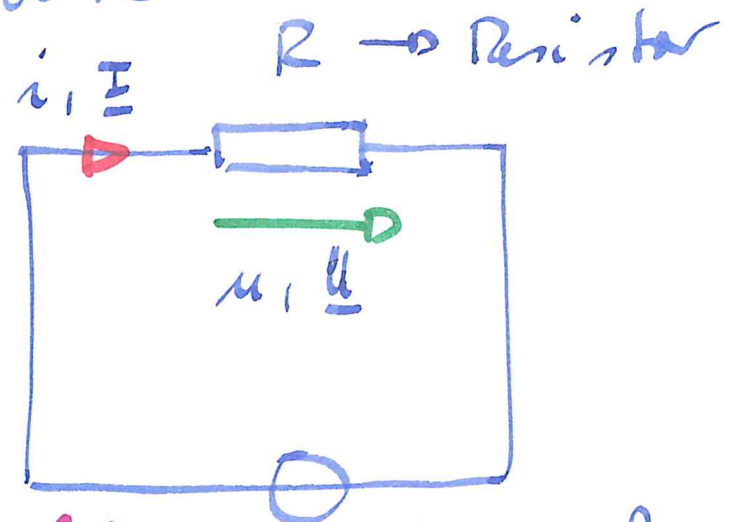

→ later

→ $U \sim i$ for ex. 250V

$$\hat{u} = 325$$

$$U = 230$$



③

$$\begin{aligned}
 u(t) &= \text{Im} \left\{ \hat{u} \cdot e^{j(\omega t + \varphi_u)} \right\} \\
 &= \text{Im} \left\{ \sqrt{2} \underline{u} e^{j\varphi_u} \cdot e^{j\omega t} \right\} \\
 &= \text{Im} \left\{ \sqrt{2} \underline{u} \cdot e^{j\omega t} \right\} \\
 &\vdots \\
 i(t) &= \text{Im} \left\{ \sqrt{2} \underline{I} e^{j\omega t} \right\}
 \end{aligned}$$

with

$$\begin{aligned}
 \underline{u} &= u \cdot e^{j\varphi_u} \\
 \underline{I} &= I e^{j\varphi_i}
 \end{aligned}$$

$$\omega = 2\pi \cdot f$$

④

$$\begin{aligned}
 u(t) &= \text{Im} \left\{ \underline{u} \sqrt{2} e^{j\omega t} \right\} \\
 i(t) &= \text{Im} \left\{ \underline{I} \sqrt{2} e^{j\omega t} \right\}
 \end{aligned}$$

OHM's law: $\underbrace{u}_{\text{DC}} = R \cdot \underbrace{I}_{\text{AC}}$


if we have a current $i(t)$:

$$\begin{aligned}
 u(t) &= R \cdot i(t) = R \cdot \text{Im} \left\{ \underline{I} \sqrt{2} e^{j\omega t} \right\} \\
 &= \text{Im} \left\{ \sqrt{2} \underbrace{\underline{I} \cdot R}_{\underline{u}} e^{j\omega t} \right\} = u
 \end{aligned}$$

$$\underline{u} = R \underline{I}$$

OHM's law by AC

- L to alternating voltage source

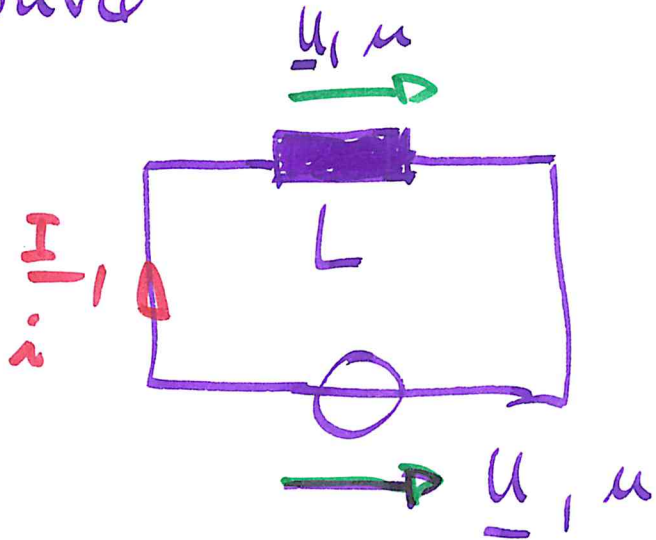

if we have a current $i(t)$:

$$u(t) = L \frac{di}{dt} = L \frac{d}{dt} \left(\text{Im} \left\{ \sqrt{2} \underline{I} e^{j\omega t} \right\} \right)$$

$$= \text{Im} \left\{ \sqrt{2} L \underline{I} \frac{d}{dt} (e^{j\omega t}) \right\} =$$

⑥

$$\begin{cases} \frac{d}{dt} (e^{2t}) = 2e^{2t} \\ f(x) = e^{2x}; f'(x) = 2 \cdot e^{2x} \end{cases}$$

$$= \text{Im} \left\{ \sqrt{2} L \underline{I} j\omega \cdot e^{j\omega t} \right\}$$

\underline{u}


$$\underline{u} = j\omega L \underline{I}$$

Example: $L = 10 \text{ mH}$

$$\underline{u} = 230 \text{ V } e^{j40^\circ}, 50 \text{ Hz}$$

Calc: $\underline{I} = ?$
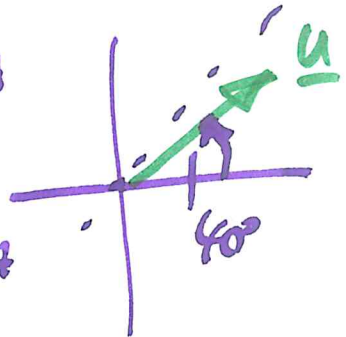
$$\underline{u} = j\omega L \underline{I}; \underline{I} = \frac{\underline{u}}{j\omega L}$$



$$\underline{\underline{I}} := \frac{230V \cdot e^{j40^\circ}}{j \cdot 2\pi \cdot 50 \text{ Hz} \cdot 10 \text{ mH}} =$$

$\left. \begin{array}{l} \text{Hz} = \frac{1}{\text{s}} \\ \text{H} = \frac{\text{Vs}}{\text{A}} \end{array} \right\} \text{!}$

$$= \frac{230V \cdot e^{j40^\circ} \cdot A}{j \cdot 2\pi \cdot 50 \cdot 10 \cdot 10^{-3} \text{ Vs}}$$

$\left. \begin{array}{l} j = 0 + 1j = 1 \cdot e^{j90^\circ} \\ \uparrow \quad \uparrow \\ \text{kantenian f.} \end{array} \right\} \rightarrow j = e^{j90^\circ}$

$$= \frac{230V \cdot e^{j40^\circ} \cdot A \cdot 10^3}{e^{j90^\circ} \cdot 314 \cdot 10} = 73.25A \cdot e^{-j50^\circ}$$

⑦

⑧

