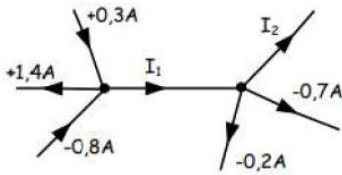



Question 1 (10 P)

- Calculate the currents I_1 and I_2
- For the right node change if necessary the directions of the currents, so that in the circuit diagram only positive numbers (currents) appear, and sketch the circuit diagram.



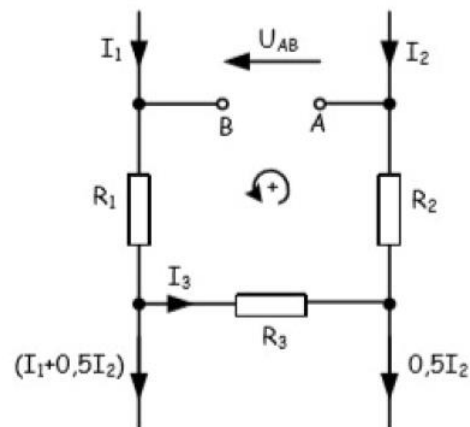Question 2 (10 P)

The current I_3 and the voltage U_{AB} have to be calculated. There is no current flowing through terminals AB. $I_1 = 14 \text{ A}$; $I_2 = 6.4 \text{ A}$; $R_1 = 20 \Omega$; $R_2 = 17 \Omega$; $R_3 = 6 \Omega$




Question 3 (15 P)

You have four resistors of $20 \text{ k}\Omega$ each.

- Calculate the equivalent resistance, if all resistors are connected in parallel.
- Calculate the equivalent resistance, if all resistors are connected in series.
- How should the four resistors be connected (draw the circuit), so that the total resistance is $20 \text{ k}\Omega$?

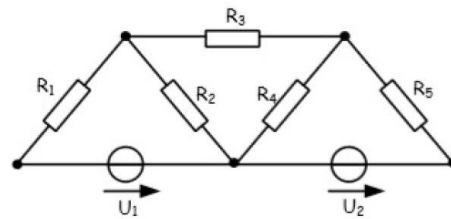Question 4 (25 P)

Calculate the unknown currents. To do this, set up the linear equation system in matrix form (with numerical values)



Question 5 (10 P)

- The resistor R , the resistors $2R$, $4R$ and $8R$ are connected in parallel. How big must R be chosen, so that the total resistance $R_t = 1 \text{ k}\Omega$.
- Sketch a circuit diagram first.

Question 6 (20 P)


The figure below shows the characteristic of a voltage source.

A)

- Calculate the internal resistance R_i .
- Calculate the short-circuit current I_s .

B)

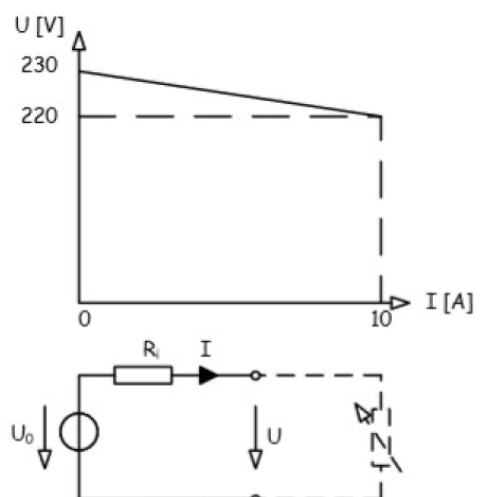- How does the terminal voltage U depend on the current I ? $U(I) = ?$ (Formula)
- Draw the curve of your calculated formula in Ba). Then label the points of intersection.



Question 7 (25 P)

A winding is rotating in homogen magnetic field, see the sketch right.

- Calculate the magnetix flux through the winding, depending from the angle α of the winding area to the magnetic field strength
- Show, that the voltage at the ends of the winding is sinusoidal (mathematical).

