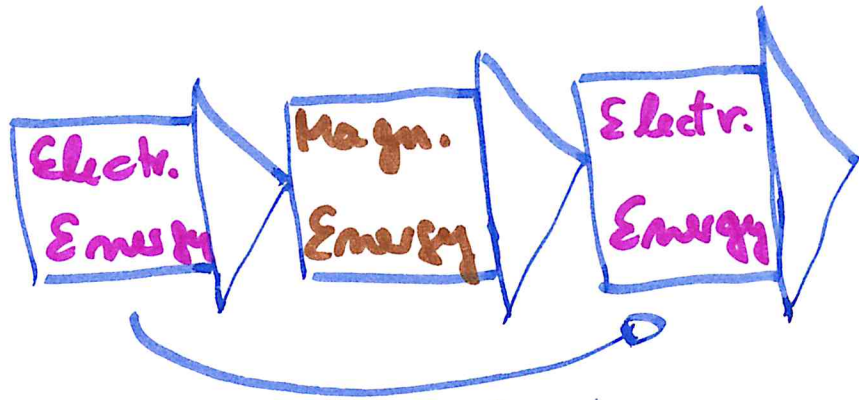


8th January 2020, Rezekne

Electrical Machinery

The Transformer (Tr.)



no wired
connection

⇒ our high standard of living depends high on electrical energy everywhere

①

②

⇒ electrical power supply depends high on transformers. Electrical power supply without transformers is not possible (I cannot imagine)

⇒ Picture Voltage level

⇒ Voltage levels (in μV)

380 μV Highest vol

110 μV High voltage

20 μV Middle vol.

230/400V Low voltage


⊕

③

This is not possible without transformers


Transformers → ideal Tr. (1.)
 → real Tr. (2.)

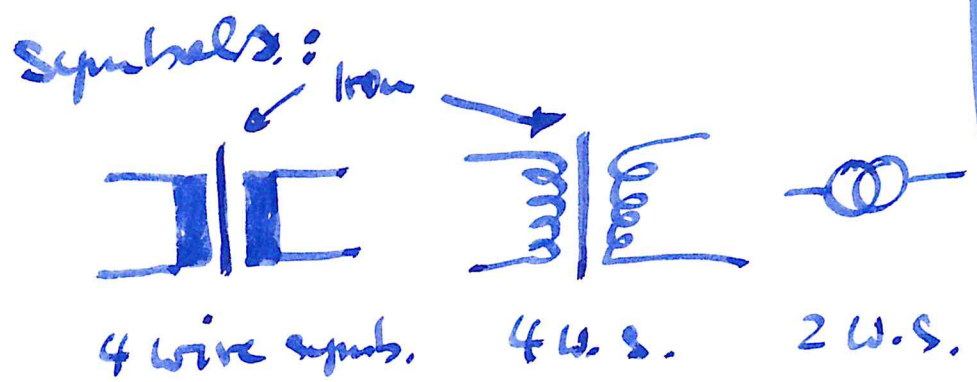- ideal transformer
 - ≡ no losses
 - ≡ $\mu_r \rightarrow \infty$
 - ≡ no magnetic leakage flux



④

physical model

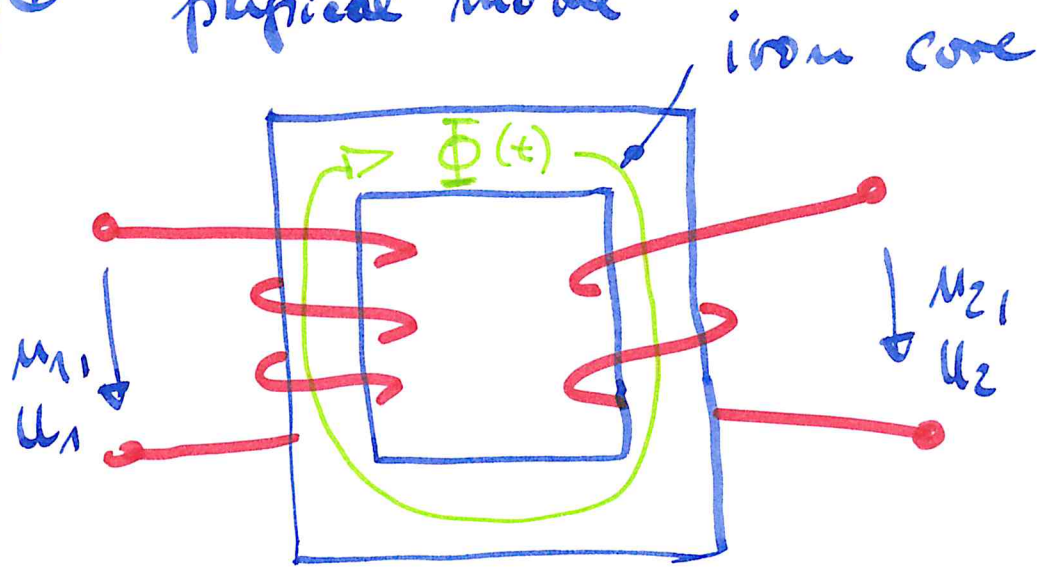

coil with N_1 wind. coil with N_2 wind.

We suppose, that inside the iron core is a magnetic flux $\Phi(t) \neq \text{const}$ ("God made the flux")

If there is magnetic flux, then at the coils are voltages with the induction law:

$$u_1 = N_1 \cdot \frac{d\Phi}{dt}$$

$$u_2 = N_2 \cdot \frac{d\Phi}{dt}$$

$$\frac{u_1}{N_1} = \frac{d\Phi}{dt} = \frac{u_2}{N_2} \quad ; \quad \frac{u_1}{N_1} = \frac{u_2}{N_2}$$

$$(1) \quad \frac{u_1}{u_2} = \frac{N_1}{N_2} = \ddot{u} = t$$

t : transmission ratio

Voltage transforming law of an ideal Tr.

(5)

(6)

ideal Tr. \rightarrow no losses $\Rightarrow P_1 = P_2 \Rightarrow u_1 \cdot I_1 = u_2 \cdot I_2$

$$\frac{I_2}{I_1} = \frac{u_1}{u_2} = t$$

(2)

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = t$$

Current transforming law of an ideal Tr.


$$(1) * (2) \Rightarrow \frac{u_1}{u_2} \cdot \frac{I_2}{I_1} = t^2$$

$$\frac{u_1 / I_1}{u_2 / I_2} = \frac{z_1}{z_2} = t^2 \quad (3)$$

Impedance transmission of an ideal Tr.

Examples

1

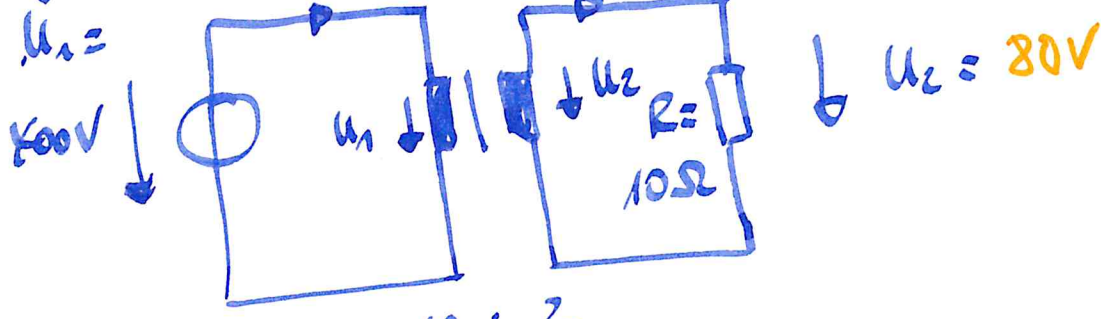


$10 : 2$
 $\Rightarrow t = 5$

$\frac{u_1}{u_2} = \frac{N_1}{N_2} = 5$; $u_2 = \frac{u_1}{5} = 80V$

$I_2 = \frac{u_2}{R} = \frac{80V}{10\Omega} = 8A$

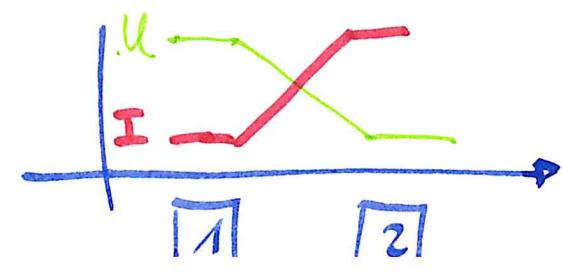$\frac{I_2}{I_1} = t = 5$; $I_1 = \frac{I_2}{5} = 1.6A$




7

8

$P_1 = u_1 I_1 = 640W$
 $P_2 = u_2 I_2 = 10 \times 640 = 640W$

2

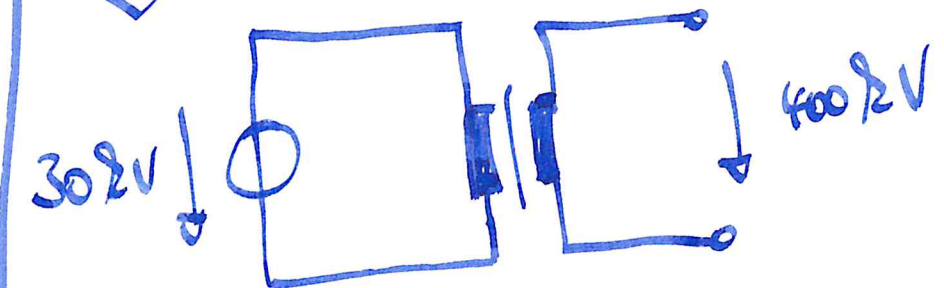


$500 : N_2 = ?$

$\frac{u_1}{u_2} = \frac{N_1}{N_2}$; $N_2 = N_1 \frac{u_2}{u_1} = \frac{400\Omega}{300V}$

$N_1 = \frac{40}{3} = 13.33$
 $= 6666.7$

3

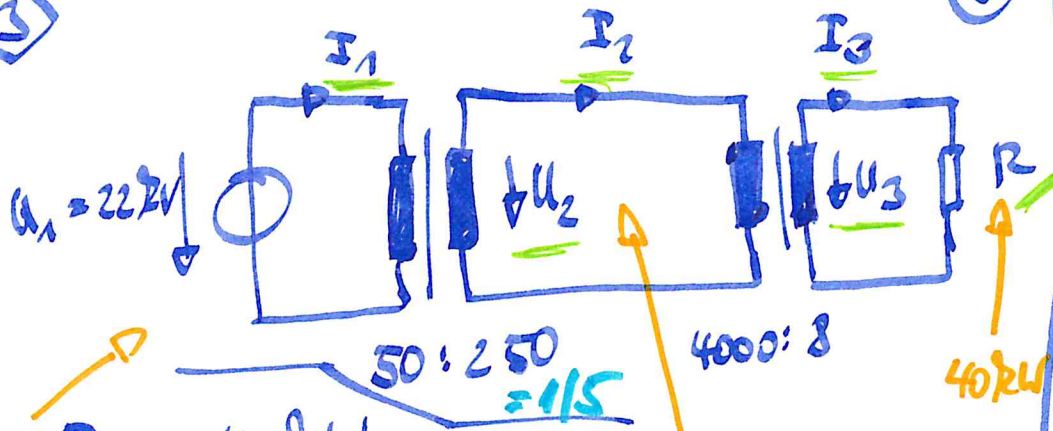

9

10

$$\frac{I_3}{I_2} = \frac{4000}{8} = 500 ; I_3 = 0.36A$$

$$I_3 = 180 A \cdot 500$$

$$P_3 = P = 40 kW = U_3 \cdot I_3$$

$$U_3 = \frac{40 kW}{180 A} = 222 V$$

* $P_R = P_3 = 40 kW$ by 220V

$$P = U \cdot I = I^2 \cdot R = \frac{U^2}{R}$$

$$\Rightarrow R = \frac{U^2}{P} = \frac{(220V)^2}{40 kW}$$

$$= 1.21 \Omega$$

$$P(222V) = \frac{(222V)^2}{1.21 \Omega} =$$

$$I_1 = \frac{P_1}{U_1} = \frac{40 kW}{22 kV} = 1.8 A$$

$$\frac{U_1}{U_2} = \frac{N_1}{N_2} = \frac{50}{250} = \frac{1}{5} ; U_2 = U_1 \cdot 5 = 110 kV$$


$$\frac{I_2}{I_1} = \frac{1}{5} ; I_2 = \frac{I_1}{5} = 0.36 A$$

$$I_2 \cdot U_2 = P_2 = P ; I_2 = \frac{P_2}{U_2} = \frac{40 kVA}{110 kV} = 0.36 A$$

$40 kW$ $P_R = 40 kW$
(by ~~$U_3 = 220V$~~)

$40 kW$

$40 kW$

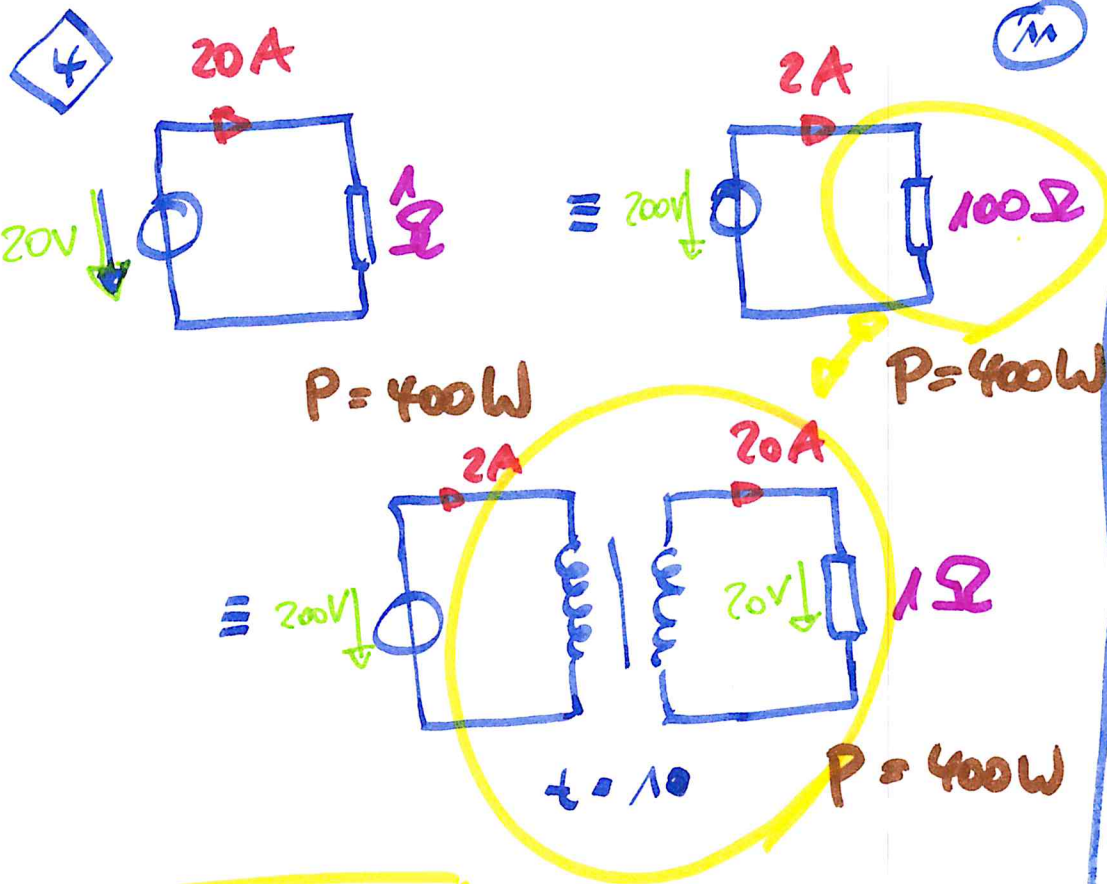




$$\frac{z_1}{z_2} = t^2$$


$$z_1 = z_2 \cdot t^2$$

$$= 1\Omega \cdot 10^2$$

$$= 100\Omega$$

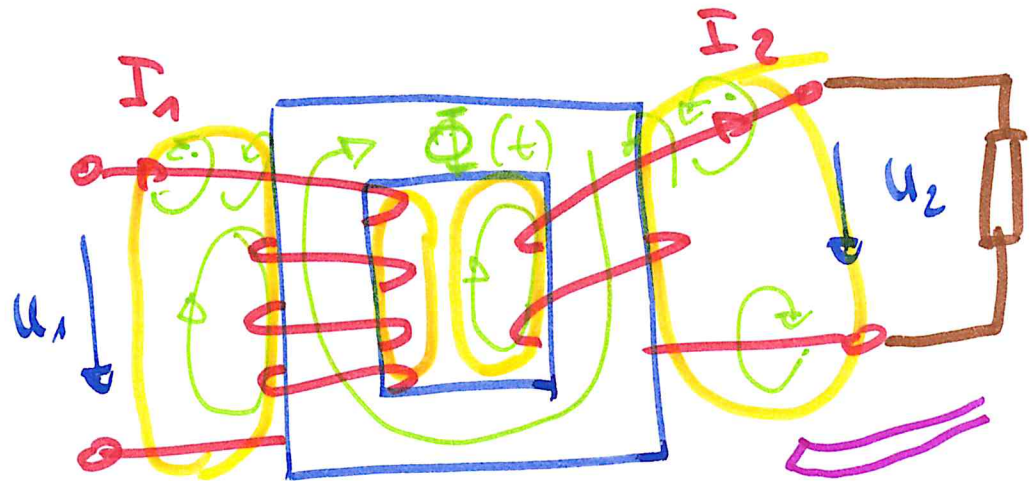Example for transforming impedances

- ⑫
- real transformer
 - has losses ($P = I^2 \cdot R$)
 - has hysteresis 
 - leakage flux 
 - eddy currents 
- flux: $\Phi = L \cdot I$




leakage flux Φ_l

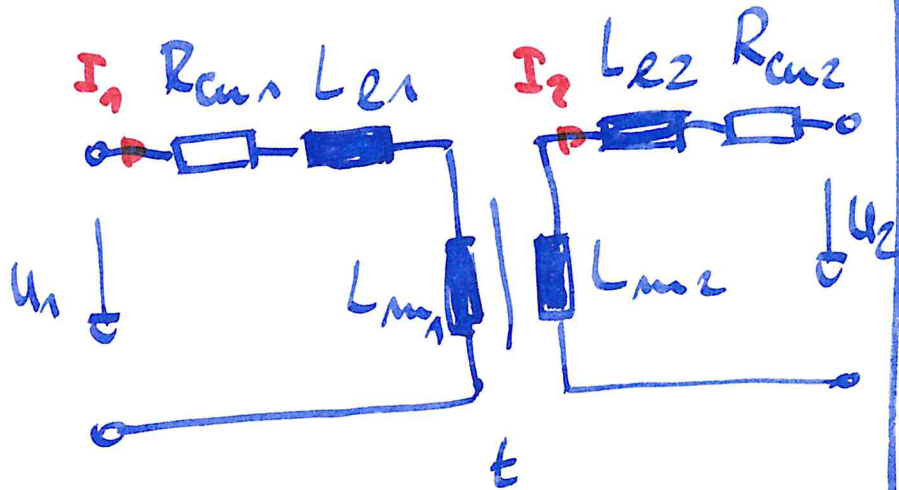(13) $L_e = \frac{\Phi_e}{I}$: leakage inductance


Φ in iron $\rightarrow \Phi_m = \Phi_{main}$

$L_m : \frac{\Phi_m}{I}$: main inductance



electric sub-circuit

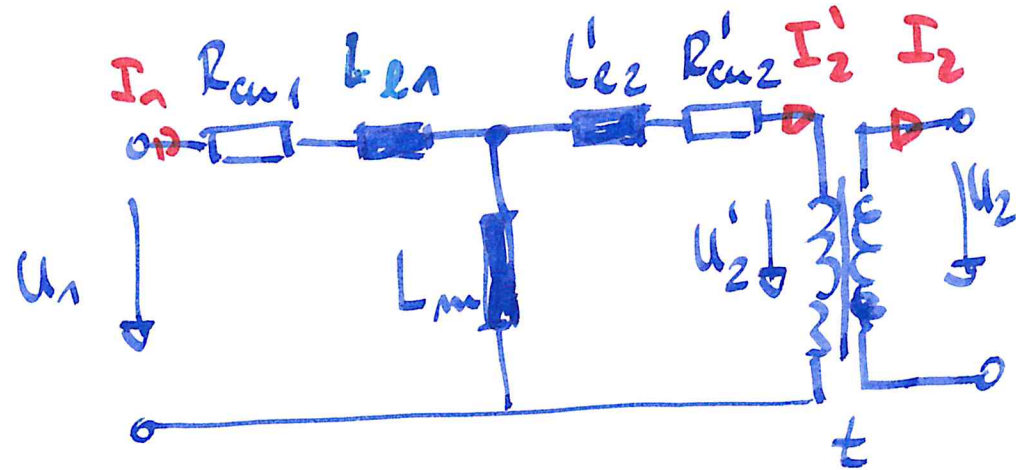(14) We bring L_{e2} and R_{cu2} to side no. 1:



ideal tr.

$$\frac{I_2}{I_2'} = t ; \frac{U_2'}{U_2} = t$$


$$I_2' = \frac{I_2}{t} ; U_2' = U_2 \cdot t$$

$$L'_{e2} = L_{e2} \cdot t^2$$

$$R'_{cu2} = R_{cu2} \cdot t^2$$

full electric subcircuit for a transformer:

(15)

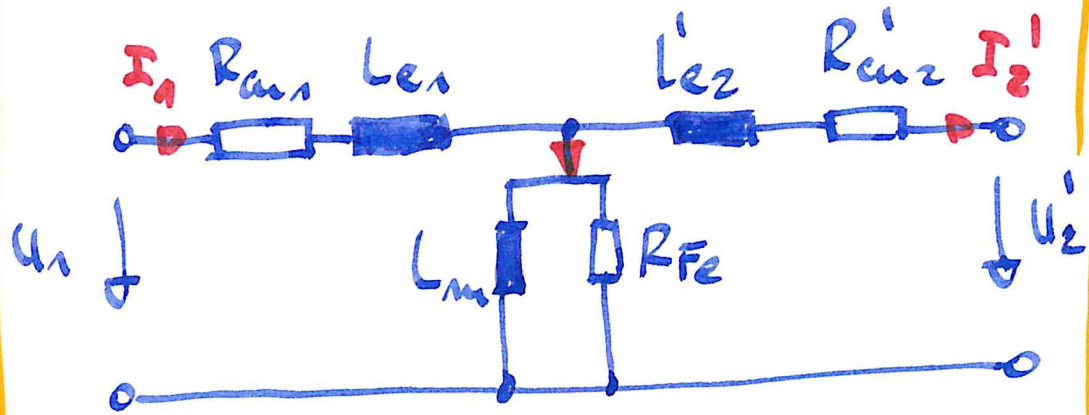

R_{Fe} : R of iron $\begin{cases} \rightarrow \text{hyst. losses} \\ \rightarrow \text{eddy current losses} \end{cases}$

$$R_{cu1}, R'_{cu2} \ll R_{Fe}$$

$$L_{e1}, L'_{e2} \ll L_m$$

(16)

ideal tr.: $R_{cu1} = R'_{cu2} = 0$

$$L_{e1} = L'_{e2} = 0$$

$$L_m \rightarrow \infty$$

$$R_{Fe} \rightarrow \infty$$

$$Z_m = \omega \cdot L_m \rightarrow \infty$$

full electric subcircuit for an ideal transformer:



$$\Rightarrow I_2' = I_1 = \frac{I_2}{t} \Rightarrow$$

$$\frac{I_2}{I_1} = t \quad (17)$$


current law
of an ideal tr.

$$\Rightarrow U_1 = U_2' = U_2 t \Rightarrow$$

$$\frac{U_1}{U_2} = t$$

voltage law
of an ideal tr.

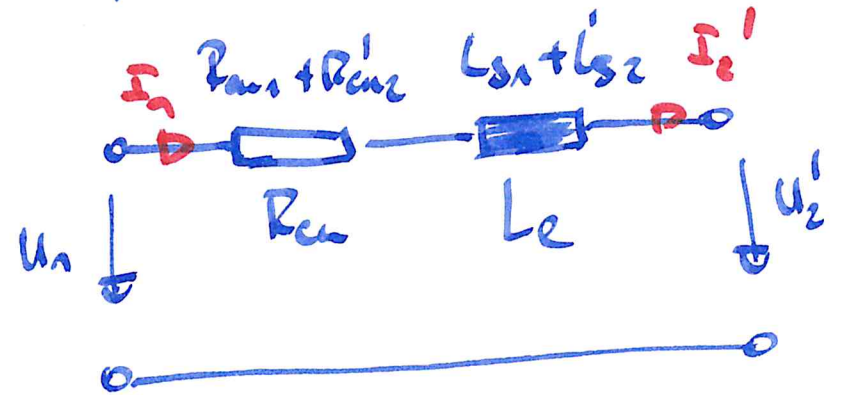\Rightarrow a transformer with full load:



\Rightarrow a transformer with no load:

