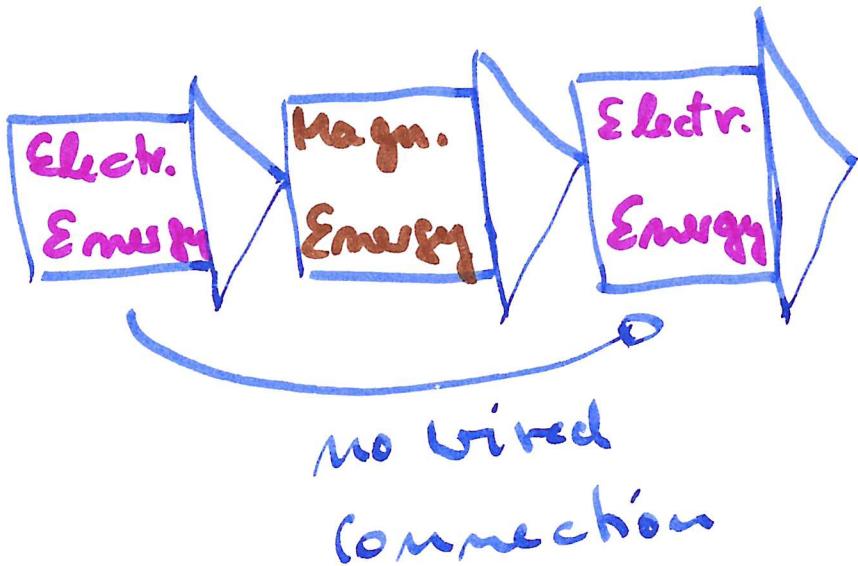


8th January 2020, Reserve

Electrical Machinery

The Transformer (Tr.)



=> our high standard of living depends high on electrical energy everywhere

①

②

=> electrical power supply depends high on transformers. Electrical power supply without transformers is not possible (I cannot imagine)

=> Picture Voltage levels

=> Voltage levels (in Sr.)

380 kV highest volt.

110 kV High voltage

20 kV Middle volt.

230/400 V Low voltage

④
This is not possible without
transformers

Transformers \rightarrow ideal Tr. (1.)
 \rightarrow real Tr. (2.)


- ideal transformer
 - $\hat{=}$ no losses
 - $\hat{=}$ $\mu_r \rightarrow \infty$
 - $\hat{=}$ no magnetic leakage flux

Symbols:



4 wire symb. 4 W.S. 2 W.S.

physical model

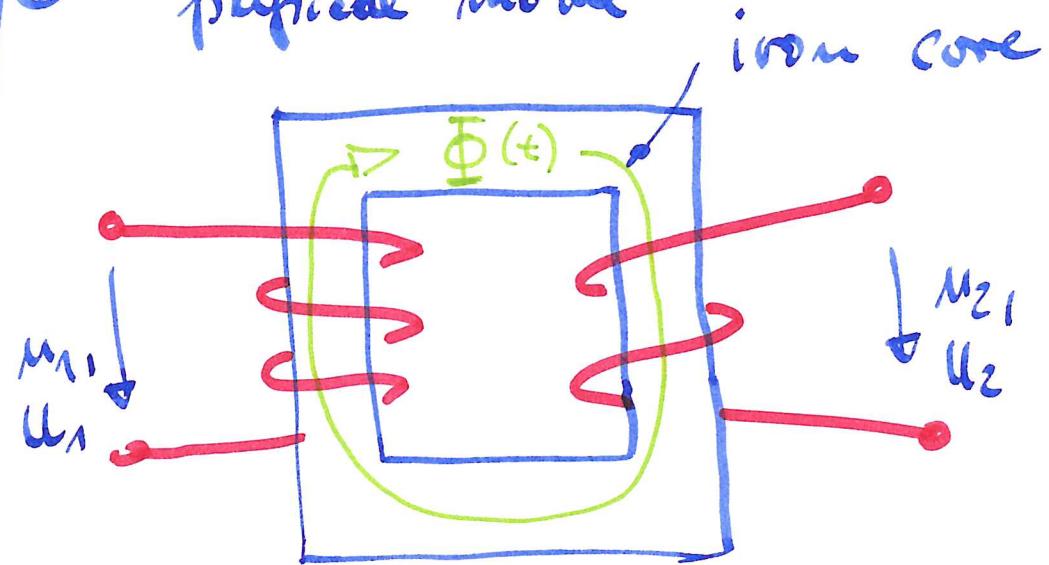

coil with N_1 wind.
coil with N_2 wind

We suppose, that inside the iron core is a magnetic flux $\Phi(t) \neq \text{const}$ ("God made the flux")

If there is magnetic flux,
then at the coils are voltages with
the induction law:

$$U_1 = N_1 \cdot \frac{d\Phi}{dt}$$

$$U_2 = N_2 \cdot \frac{d\Phi}{dt}$$

$$\frac{U_1}{N_1} = \frac{d\Phi}{dt} = \frac{U_2}{N_2} \quad ; \quad \frac{U_1}{N_1} = \frac{U_2}{N_2}$$

$$(1) \quad \frac{U_1}{U_2} = \frac{N_1}{N_2} = t = \ddot{\nu}$$

t : transmission
 \Rightarrow ratio

Voltage
transfor-
muring
law of
an ideal

⑤

⑥

ideal Tr. \rightarrow no losses \Rightarrow

$$P_1 = P_2 \Rightarrow$$

$$U_1 I_1 = U_2 I_2$$

$$\frac{I_2}{I_1} = \frac{U_1}{U_2} = t$$

(2)

$$\frac{I_2}{I_1} = \frac{N_1}{N_2} = t$$

|| Current transforming law of
an ideal Tr.

(1) * (2) \Rightarrow


$$\frac{U_1}{U_2} \cdot \frac{I_2}{I_1} = t^2$$

$$\frac{U_1 / I_1}{U_2 / I_2} = \frac{z_1}{z_2} = t^2$$

③

Impedance transmission of
an ideal Tr


Exemplar

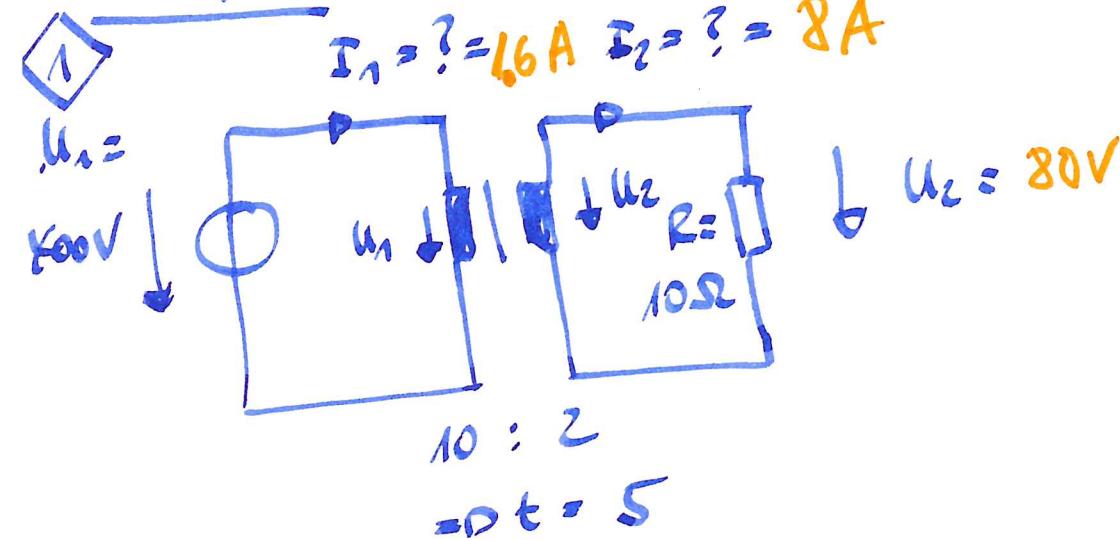

$$\frac{U_1}{U_2} = \frac{N_1}{N_2} = 5 ; \quad U_2 = \frac{U_1}{5} = 80V$$

$$I_2 = \frac{U_2}{R} = \frac{80V}{10\Omega} = 8A$$
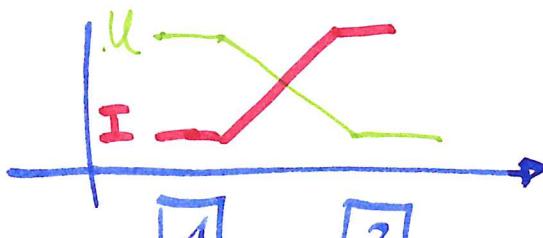
$$\frac{I_2}{I_1} = t = 5 ; \quad I_1 = \frac{I_2}{5} = 1.6A$$




⑦

⑧

$$P_1 = U_1 I_1 = 640 W$$

~~$P_2 = U_2 I_2 = 10 \cancel{A} = 640, \cancel{W}$~~

2

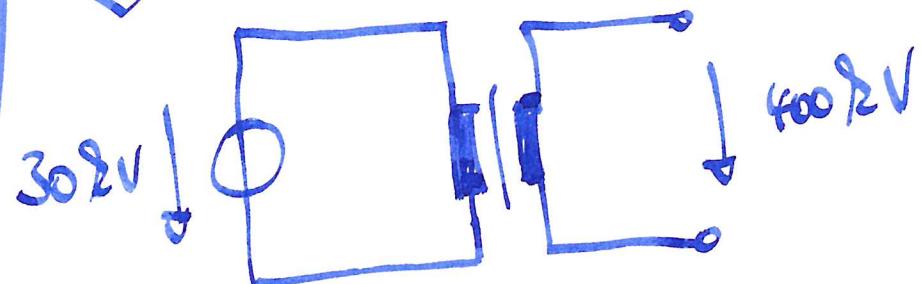


$$\frac{U_1}{U_2} = \frac{N_1}{N_2} ; \quad N_2 = N_1 \frac{U_2}{U_1} = \frac{400\Omega V}{302V}$$

$$N_1 = \frac{40}{3} = 13.33$$

$$= 6666.7$$

2

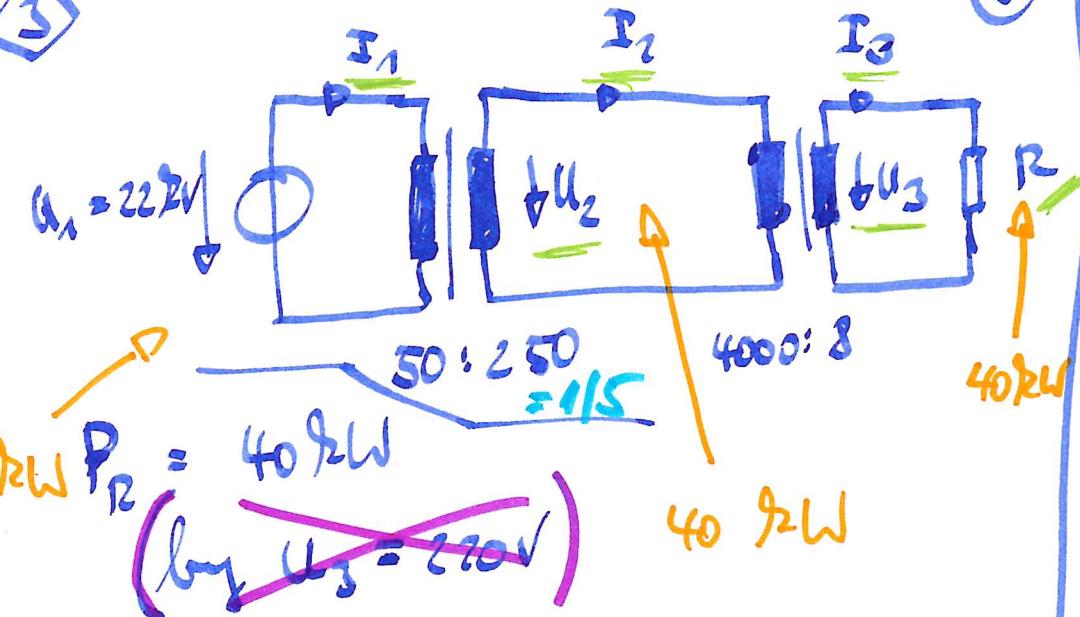

3

$$\frac{I_3}{I_2} = \frac{4000}{8} = 500; I_3 = 0.36\text{A}$$

$$I_3 = 180\text{A}$$

• 500

$$P_3 = P = 40\text{kW} = U_3 \cdot I_3$$

$$U_3 = \frac{40\text{kW}}{180\text{A}} = 222\text{V}$$


$$*) P_R = P_3 = 40\text{kW} \log 220\text{V}$$

$$P = U \cdot I = I^2 \cdot R = \frac{U^2}{R}$$

$$\Rightarrow R = \frac{U^2}{P} = \frac{(220\text{V})^2}{40\text{kW}}$$

$$= 1.21\Omega$$
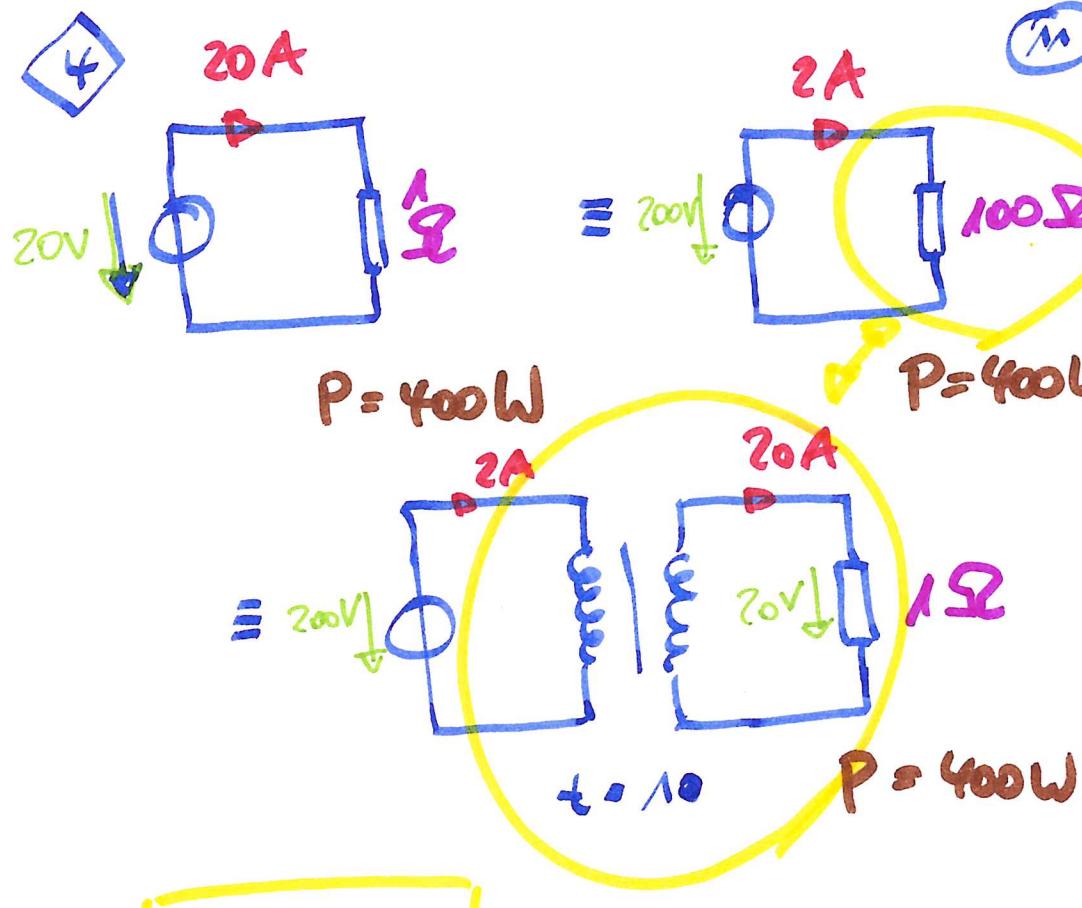
$$P(222\text{V}) = \frac{(222\text{V})^2}{1.21\Omega} =$$




Example for
transforming
impedances

$$\begin{aligned} z_1 &= z_2 \cdot t^2 \\ &= 1\Omega \cdot 10^2 \\ &= 100\Omega \end{aligned}$$

- 12
- real transformer
 - has losses ($P = I^2 \cdot R$)
 - has hysteresis
 - leakage flux
 - eddy currents

flux: $\Phi = L \cdot I$

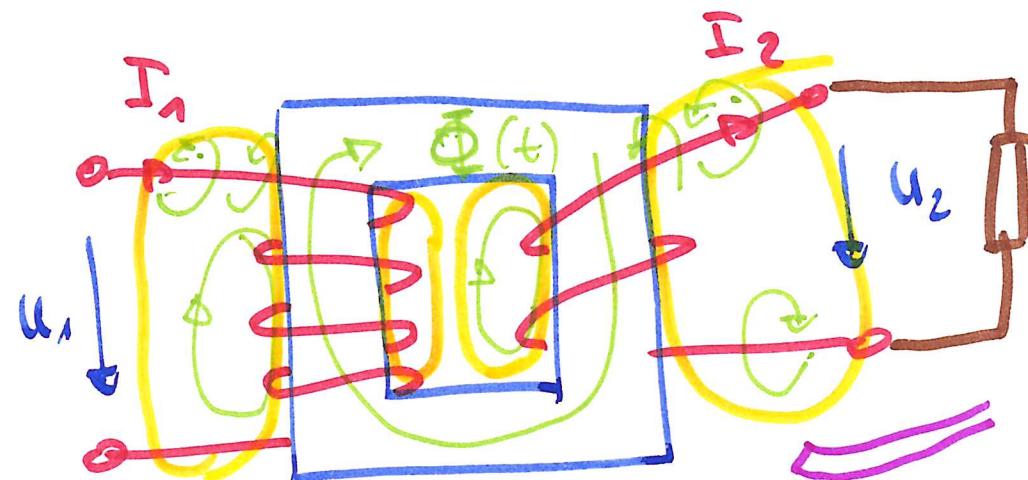


leakage flux Φ_L

$$[E_e = \frac{\Phi_e}{I}] : \text{leakage inductance}$$

$$\Phi_{\text{in iron}} \rightarrow \Phi_m = \Phi_{\text{main}}$$
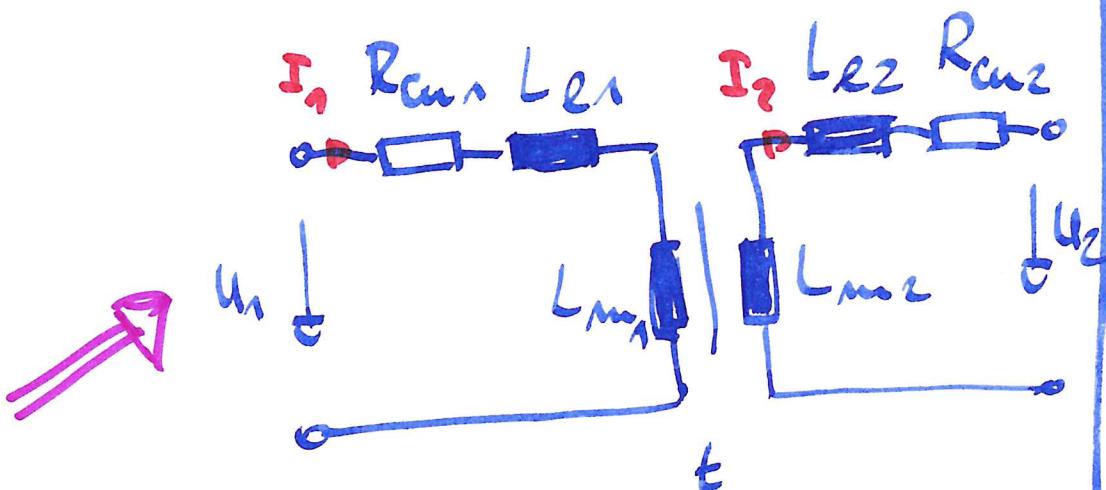
$$[L_m : \frac{\Phi_m}{I} : \text{main inductance}]$$




\hookrightarrow electric auto circuit

(13)

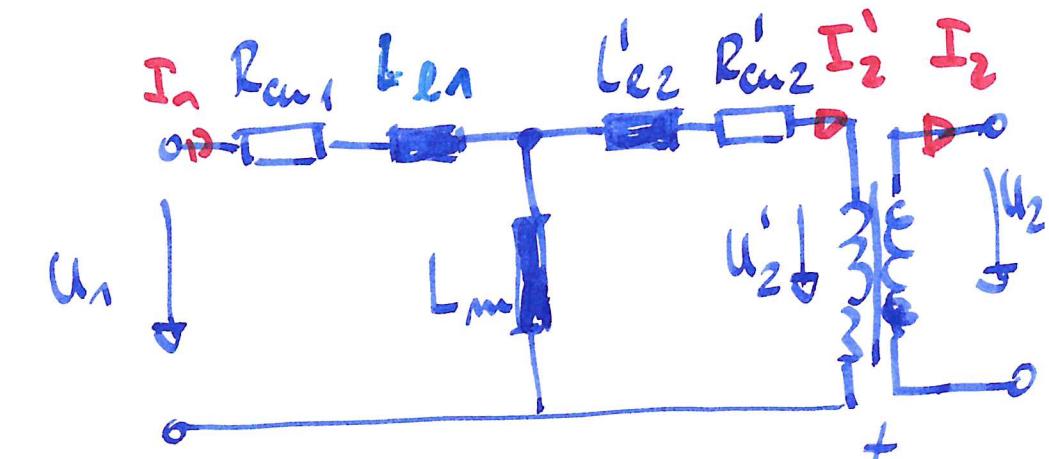(14)

we bring L_{e1} and R_{m2} to ride no. 1:



$$\frac{I_2}{I_2'} = t ; \frac{U_2'}{U_2} = t$$


$$I_2' = \frac{I_2}{t} ; U_2' = U_2 \cdot t$$

$$L_{e2}' = L_{e2} \cdot t^2$$

$$R_{m2}' = R_{m2} \cdot t^2$$

ideal tr.

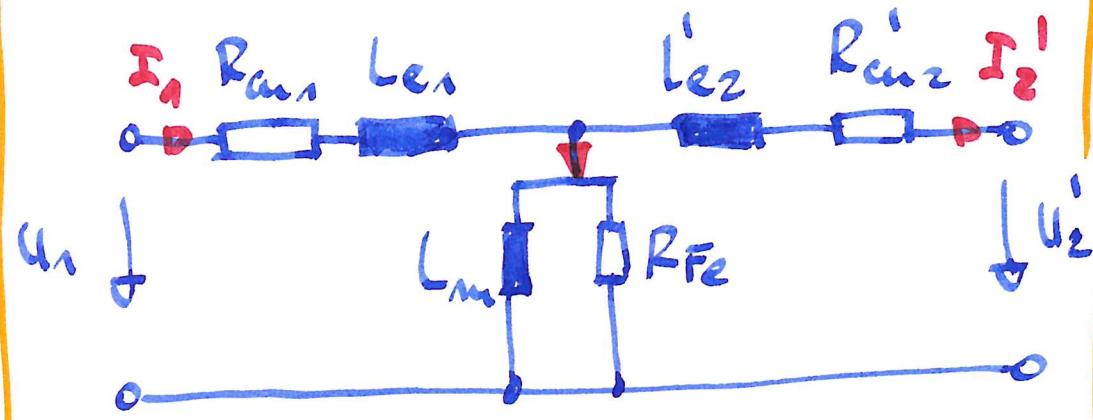full electric subcircuit for
a transformer:



R_{Fe} : R of iron → hyst. losses
→ eddy current losses

$$R_{cu1}, R_{cu2} \ll R_{Fe}$$

$$L_{e1}, L_{e2} \ll L_m$$

(16)

ideal tr.: $R_{cu1} = R_{cu2} = 0$

$$L_{e1} = L_{e2} = 0$$

$$L_m \rightarrow \infty$$

$$R_{Fe} \rightarrow 0$$

$$\left\{ z_m = \omega \cdot L_m \rightarrow \infty \right.$$

full electric subcircuit for
an ideal transformer:




$$\Rightarrow I_2' = I_1 = \frac{I_2}{t} \Rightarrow \frac{I_2}{I_1} = t \quad (13)$$

current law
of an ideal
tr.


$$\Rightarrow U_1 = U_2' = U_2 \cdot t \Rightarrow \frac{U_1}{U_2} = t$$

voltage law
of an ideal tr.

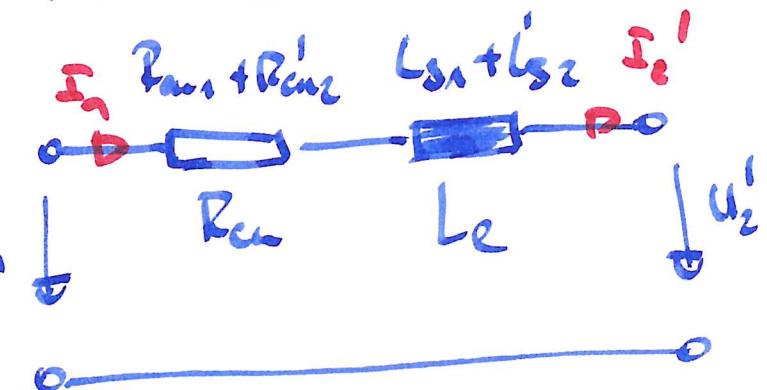\Rightarrow a transformer with
full load:



\Rightarrow a transformer with no
load:

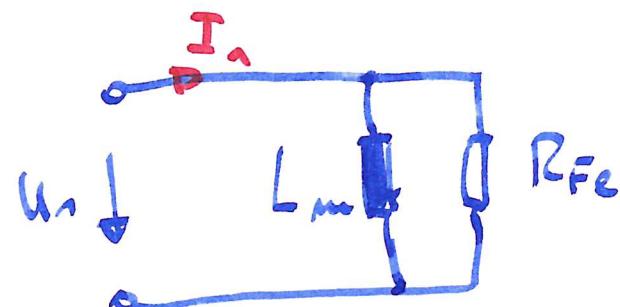


9. Jan 2020 Rechner

Electrical machinery

- 3 phase power supply

► First reason to use 3 phase P:

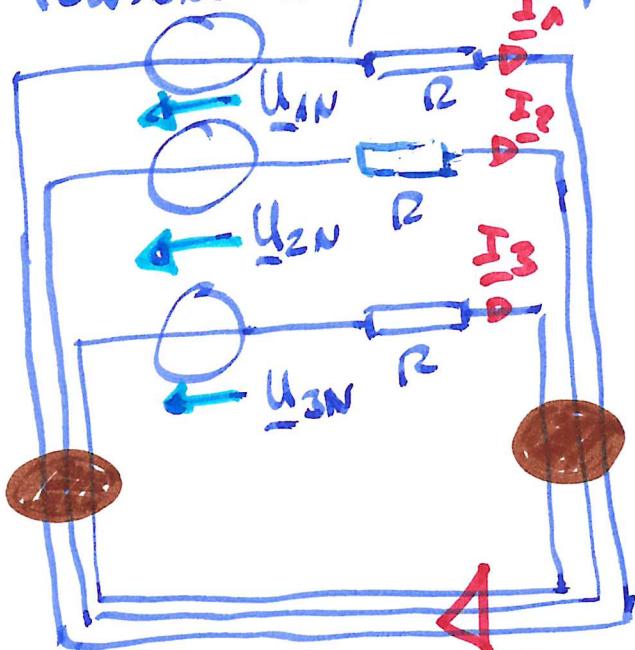


$$\underline{U}_{1N} = U_Y \cdot e^{j120^\circ}$$


$$\underline{U}_{2N} = U_Y \cdot e^{-j120^\circ} = U_Y e^{-j\frac{2\pi}{3}}$$

$$\underline{U}_{3N} = U_Y \cdot e^{-j120^\circ} = U_Y e^{-j\frac{4\pi}{3}}$$

① ②

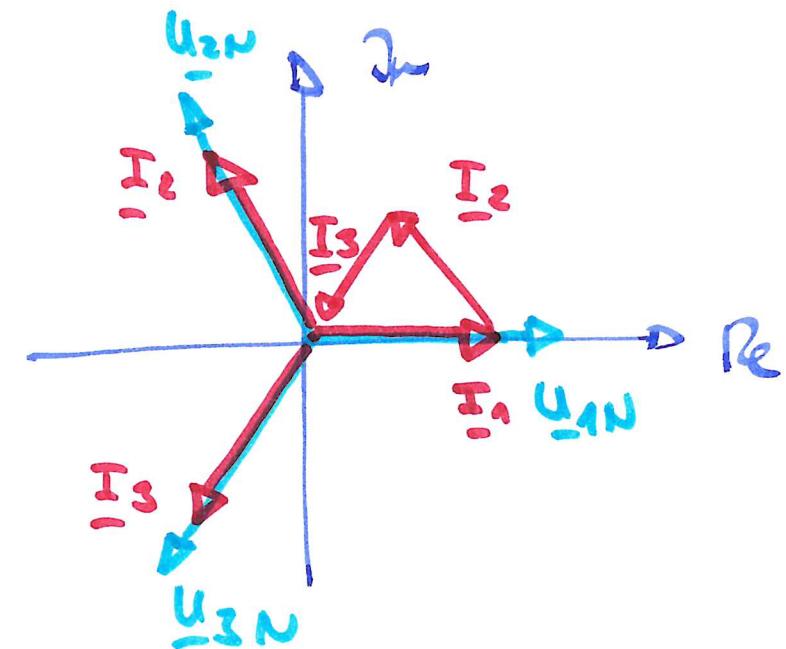
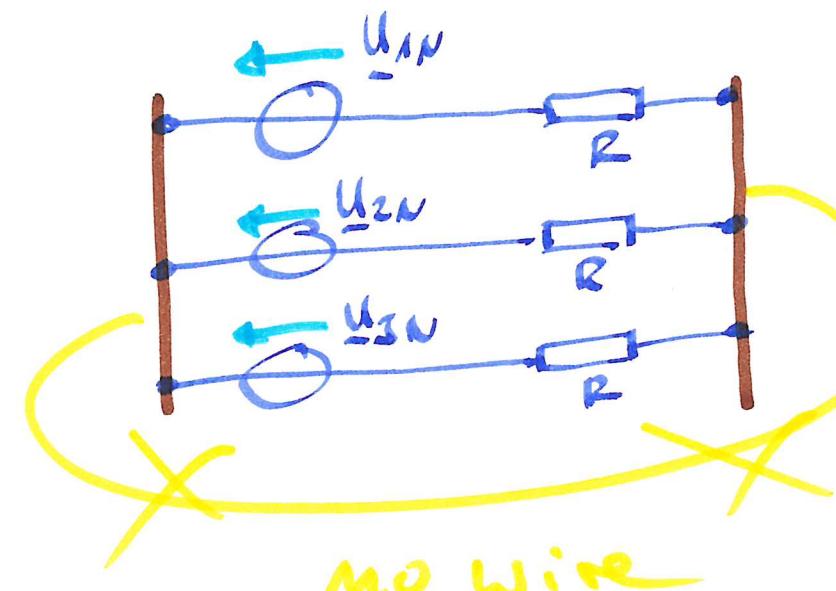
$$\text{Kirchhoff 1: } \sum_{k=1}^3 \underline{I}_k = \underline{I}_1 + \underline{I}_2 + \underline{I}_3 = 0$$




We need only the half of Leines/ copper costs


► Second reason to use 3 phase ③ power supply ④

→ we analyze the power

please see power by AC

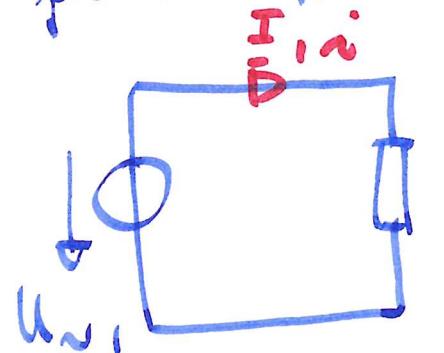

$$P = u \cdot i$$

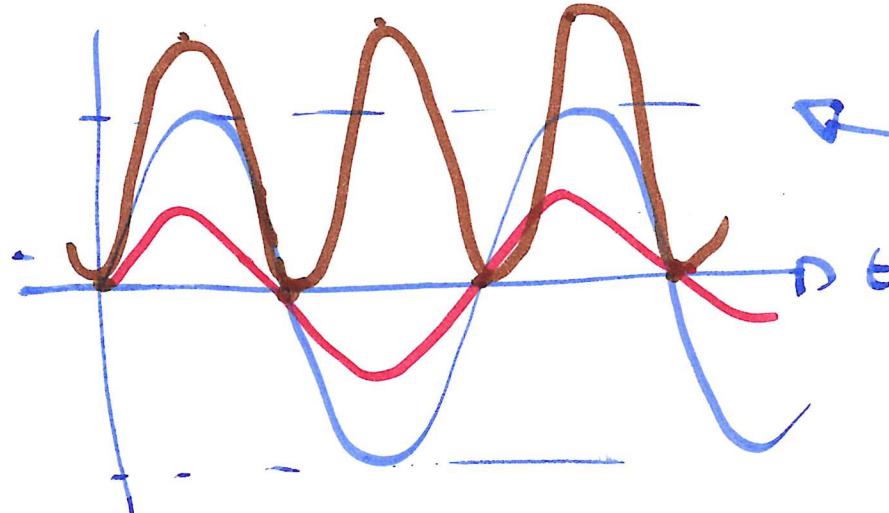

we continue in MATHCAD



→ the power of a 3 phase load (motor) is a constant, it does not depend from the time as the power in a 1 phase system

- (3 phase) synchronous machine ⑤ | ⑥

generator → (SM)
motor

► animation

3p motor / generator
1P " / "

in reality the air volume
in the motor / generator is
small, very small, all

► more real rotor (stator)

E24 pic 4


► rotating field of the stator
in case of motor

► the stator generates a
turning magnetic field
(yellow arrows). This
yellow arrows acts with
the ~~fix~~ rotor = Permanent
magnet = Electro magnet.


$$P = \omega \cdot M = \frac{C \cdot T}{\text{in}}$$

$\hookrightarrow = \text{Torque}$

n-T-diagram

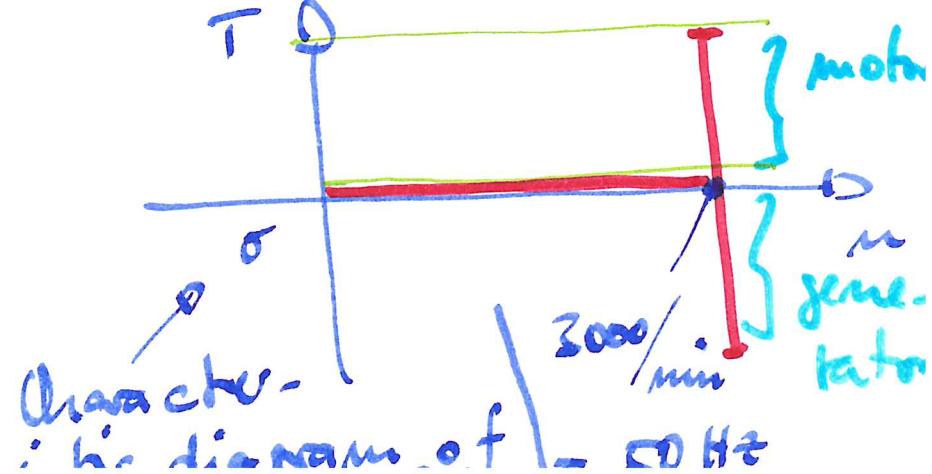


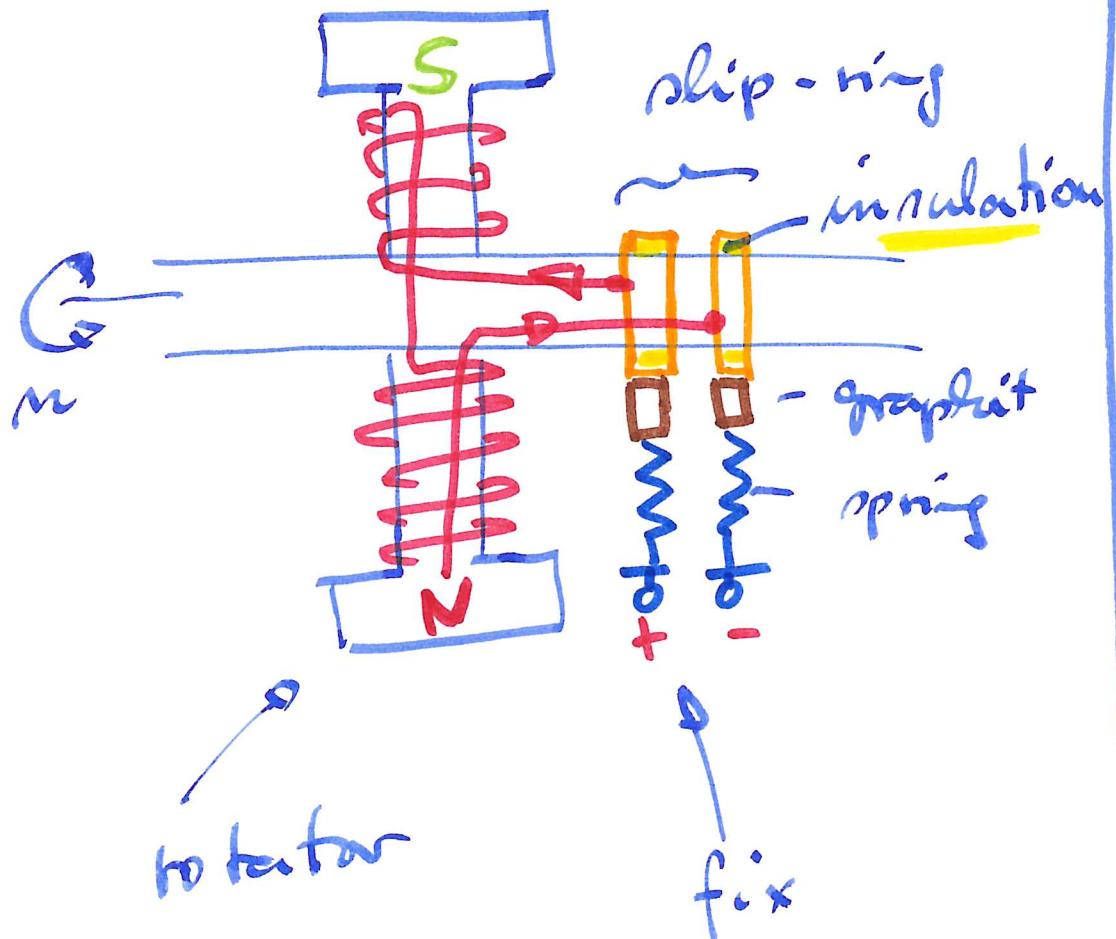to bring the current to the
turning electro magnet, you
need a slip-ring



Electrical Machinery, Rev., 11.01.20

- Look back : Synchronous motor.

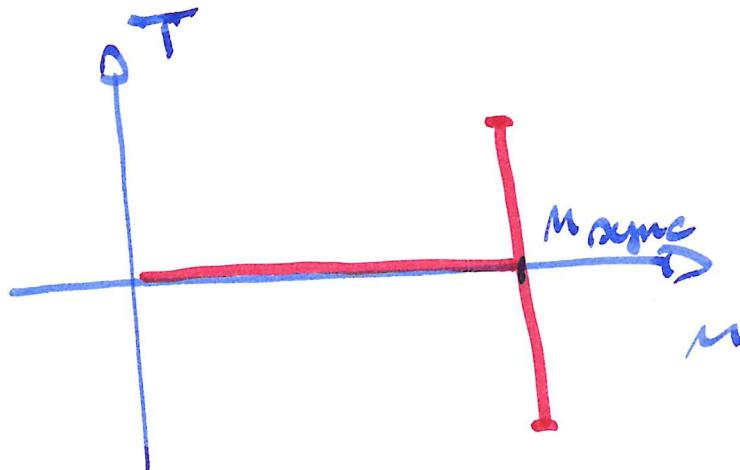

$n_{Sync} = 3000/\text{min}; 1500/\text{min};$

$1000/\text{min}; 750/\text{min} \dots$


Unit

$$n_{Sync} = \frac{f}{P}$$

number of pole pairs

$$\left\{ P = 20 \Rightarrow n_{Sync} = \frac{50}{s \cdot 20} = \frac{5 \cdot 60}{2 \text{ min}} \right.$$

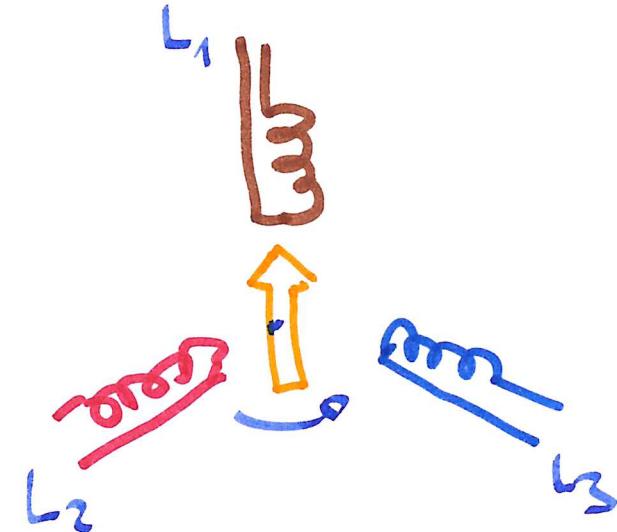
- ② • Asynchronous motor or induction motor



L_1, L_2, L_3 : 3 phase power supply




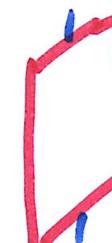rotating magnetic field
= stator field
 $= 3 \cdot n \Phi$



copper winding □

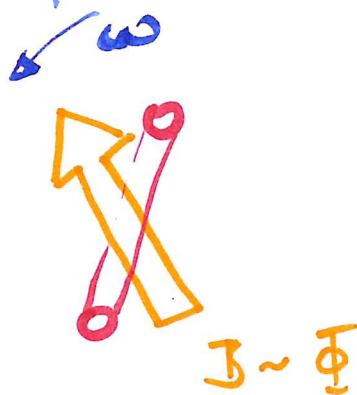We bring the copper winding into ③
the rotor field (in 2D)



$$\uparrow m_s = m_{sync}$$

$$\textcircled{P} m_w = m_{winding}$$

$$1. \text{ moment: } m_{sync} = \text{const}$$

$$m_w = 0$$

$$\Rightarrow f(i\omega) = m_s$$

$$\Rightarrow \text{big } i\omega$$

$$\Rightarrow \text{force between}$$

$$\Phi \cdot i_{11} = F_1 - F_2$$

④ 2. moment: $m_s = \text{const}$

$$m_w = m_{w2}$$

$$\Rightarrow f(i\omega) = m_s - m_w$$

$$< m_s$$

$$\Rightarrow \text{smaller } i\omega_2$$

$$\Rightarrow \text{force between}$$

$$\Phi \cdot i_{w2} = F_2 < F_1$$

\Rightarrow the winding follows the rotating field

\Rightarrow the speed of the rotor is increasing

\Rightarrow the winding begins to turn

3. moment: $M_S = \text{const}$

⑤

$$n_w = n_S$$

$$\Rightarrow f(i_w) = \sigma \quad \left(\frac{d\Phi}{dt} = 0 \right)$$

$$\Rightarrow i_{w3} = \sigma$$

$$\Rightarrow F_3 = T_3 = \sigma$$

$\Rightarrow n_w$ gets smaller


$$n_w = n_S - \varepsilon$$

4. moment: $M_S = \text{const}$

n_w = little bit smaller
than n_S but
but $\neq n_S$

$$\Rightarrow i_w > \sigma$$

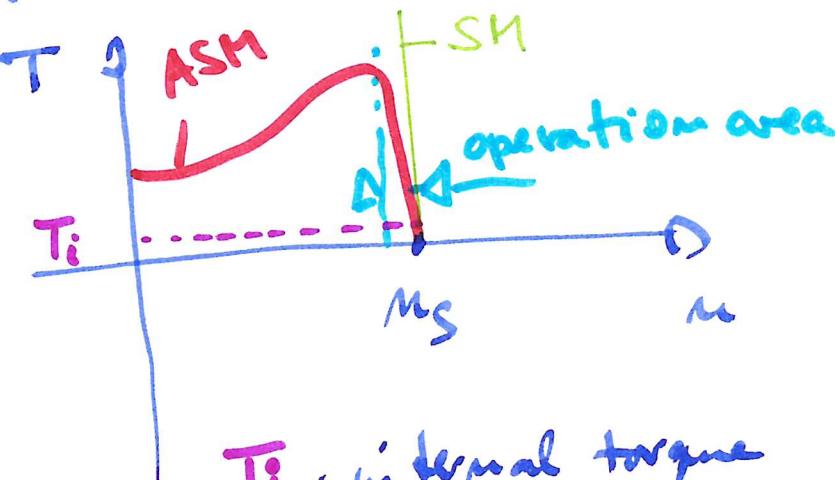characteristic diagram $T-n$
of an induction motor



T_i : internal torque
ASM are mostly used as
motors and not as gener.

ASM is the most used motor
in industry ... (in 3 phase
s.)


Real composition:
See in internet: rotor induct.
motor

You find water

- without slip rings, most by squirrel-cage motor
short circuit motor
- with slip rings (3 pieces)

each motor has internal load:

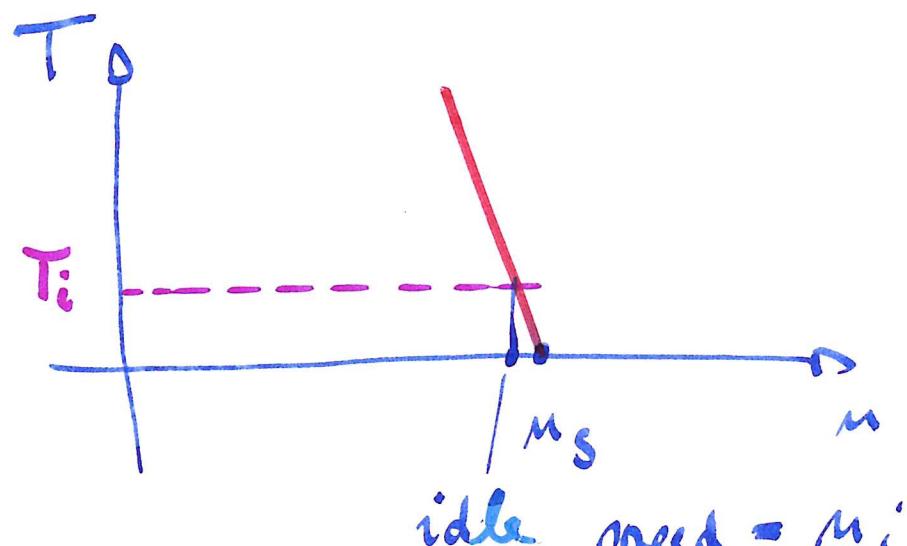- torque of the ventilation
- torque of the friction of the ball bearings



7

8

for example: $n_s = 3000/\text{min}$

$$n_i = 2800/\text{min}$$

$$n_s = 1500/\text{min}$$

$$n_i = 1480/\text{min}$$

$$p=2$$

Animation SM, ASH

www.KlemmRasten.de

- DC - machine

- animation
look our website

- script
look our website

⑨

⑩