

20. May 2019, IED - Review

## ② Industrial Electronic Devices


### Overview

- Diodes
- Bipolar transistor
- FET transistor
- Transistor (THYRISTOR)
- PV Cells (PHOTO VOLTAIC)
- OP (operational amplifier) (EUs)


①


### ② Today OP

- flexible device
- general device
- simple to handle dev.
- dev. for people without big electrical background
- :
- :

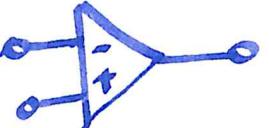Symbol:  { old }

or

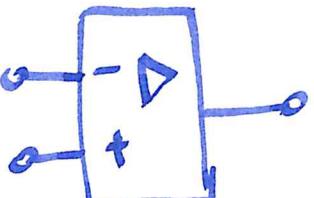 { new }

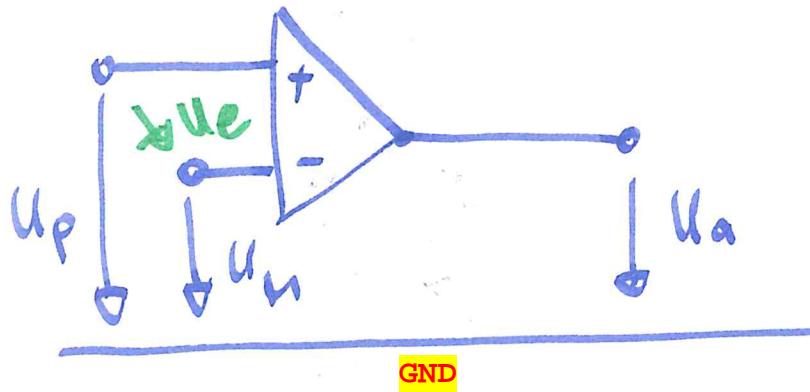

③ | K

→ What electronic circuit  
has 2000V?  $\Rightarrow$  NO!  
From where shall 2000V  
come?

Basic equation of each OP:


$$U_A = v_o (U_P - U_N) = v_o \cdot U_e$$

Example:  $U_P = 0.3V$ ;  $U_N = 0.1V$


$$v_o = 10^4 \Rightarrow \text{gain } (10^4 \dots 10^6)$$

$$U_A = 10^4 \cdot (0.3V - 0.1V)$$

$$= 10^4 \cdot 0.2V = 2000V$$

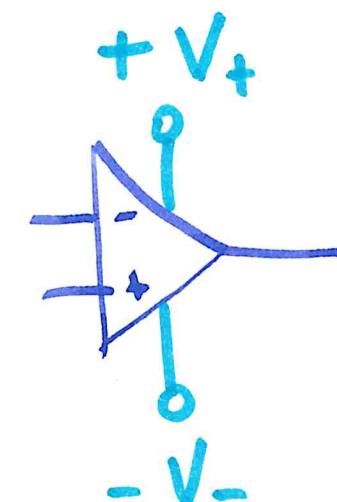

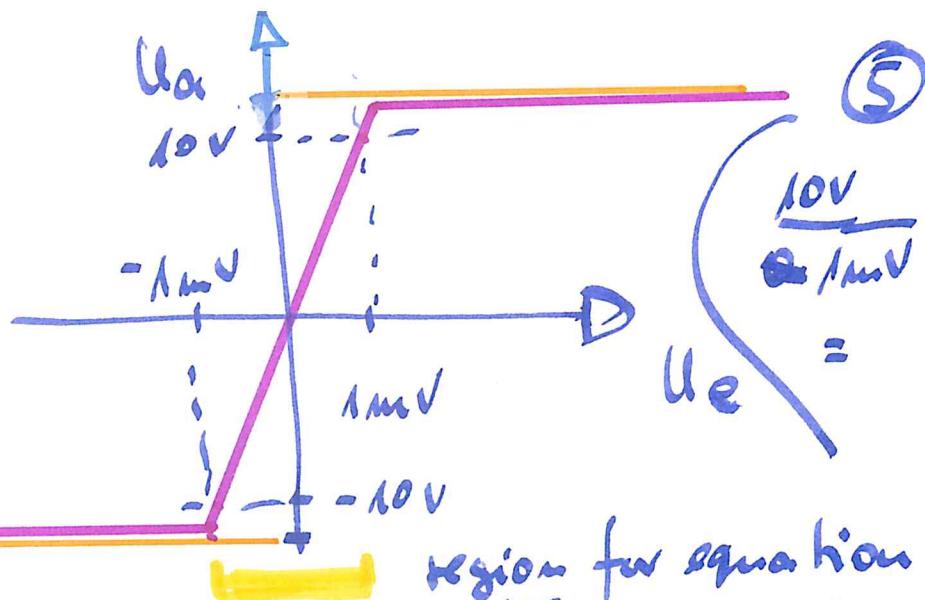$V_+$  can be  $5V \dots 10V \dots \underline{15V}$   
 $V_-$  ..  $-5V \dots -10V \dots -15V$



$$\frac{10V}{1mV} = \frac{10000 \mu V}{1 \mu V} = 10^4$$


$$V_+ = 12V ; V_- = -12V$$

↙ → characteristic diagram

> if the OP is used as an amplifier, it operates only in .

⑥ - What is in the OP? →  
see google: Inside OP  
or "Inside operational amp."  
{ lot of transistors and... }


- How it operates?

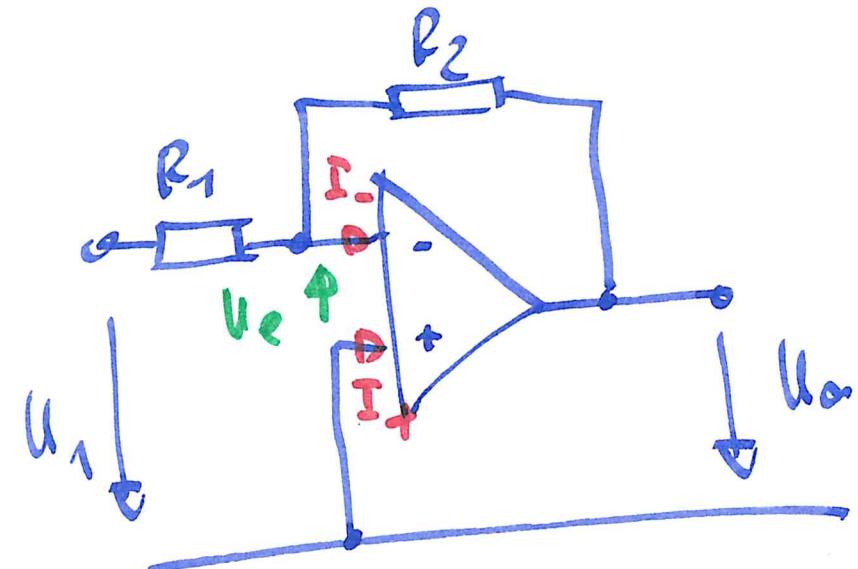

Text-book from India: ⑦ | ⑧

## Applications with OP (ideal OP)


1.) Current source?

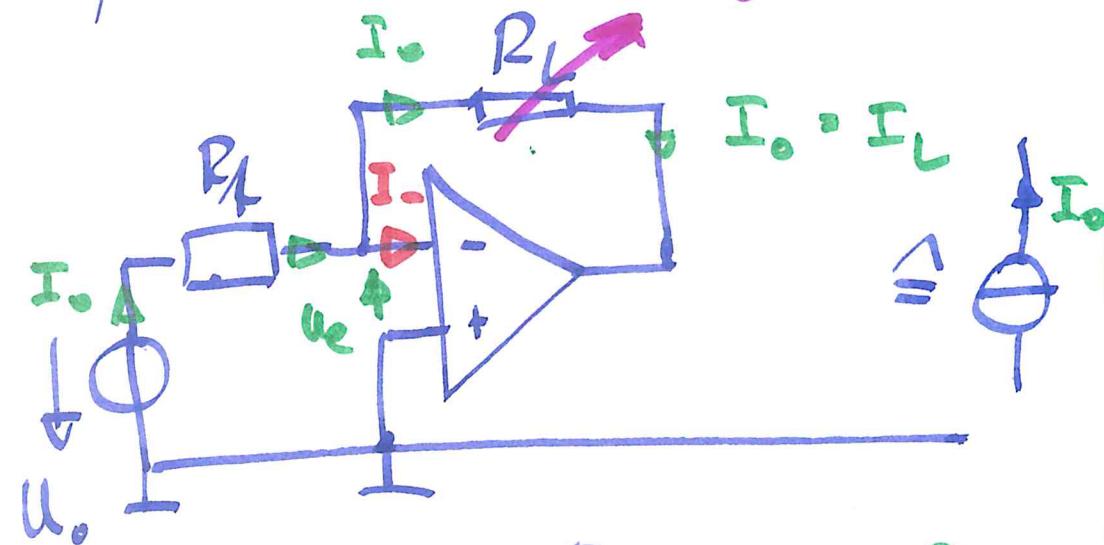


$$I_- \approx 0V \quad u_o \approx 0$$

$$I_o = \frac{u_o}{R} \xrightarrow{\text{const}} I_L = \text{const}$$

≈ const

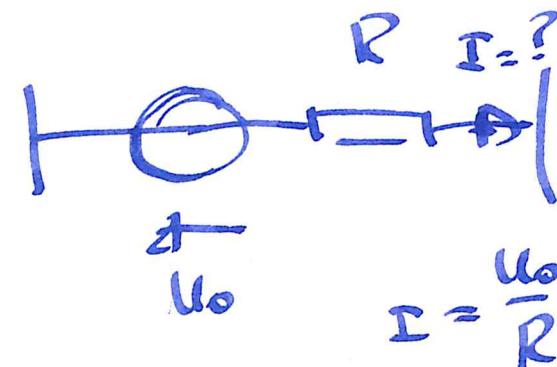


App.:

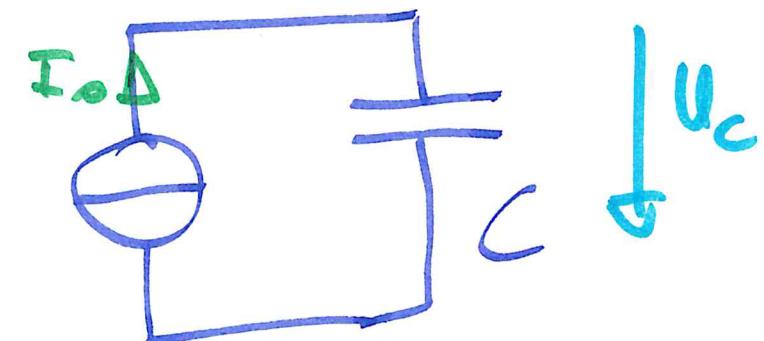

equation of C:

$$\int u = L \frac{di}{dt}$$

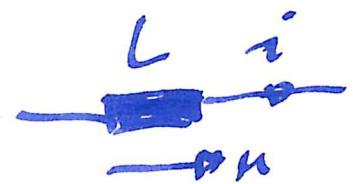


$$i = C \frac{du}{dt}$$



$$\int i dt = \int C \frac{du}{dt} dt = C \int \frac{du}{dt} dt \quad ⑨$$

$$u = \frac{1}{C} \int i dt \quad I_o$$
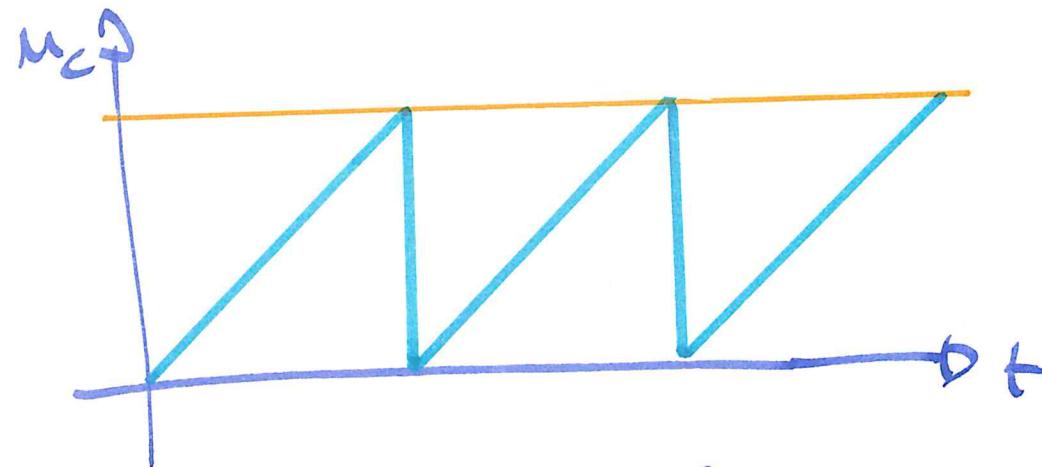
$$u = \frac{1}{C} I_o \int dt = \frac{1}{C} I_o \cdot t$$




saw-tooth -  
diagram

~~saw-tooth~~

~~saw-tooth-diagram~~

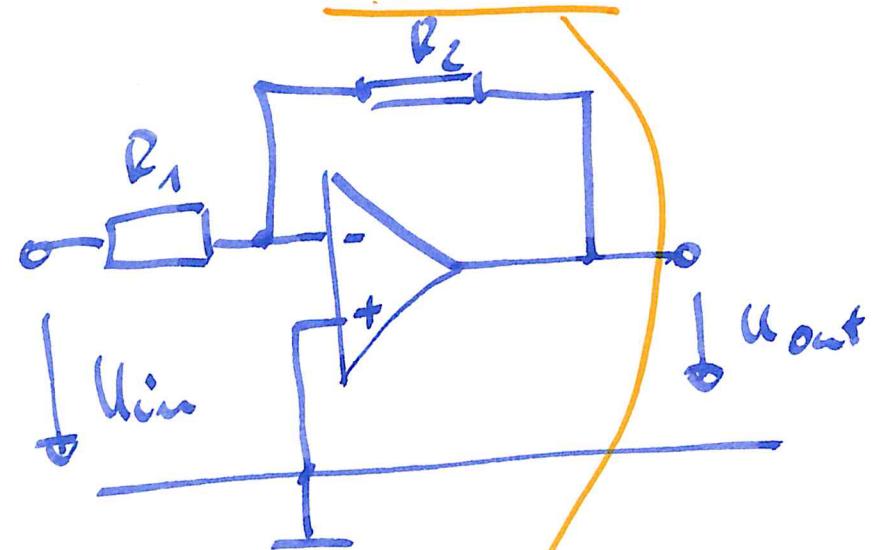⑩ 2.) ~~Si~~ Simple amplifier  
- Inverter




$$u_{out} = - \frac{R_2}{R_1} u_{in}$$

Examples: Lot of ...

3.) Impedance transformer ⑪ | ⑫ }
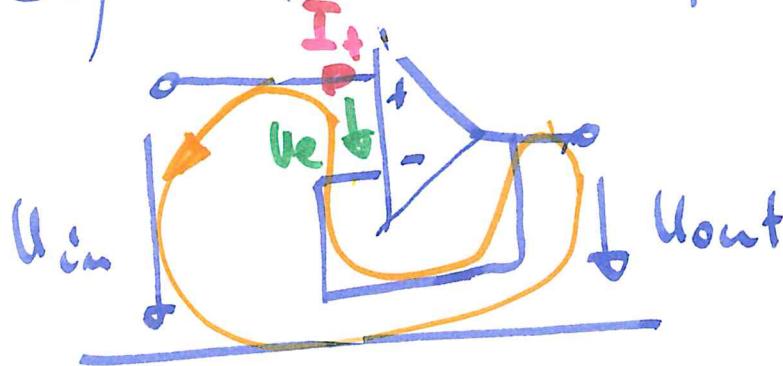
$$\frac{2 \times 2\Omega}{10^{-10} A} = \frac{2}{10^{-10}} = 2 \cdot 10^{10}$$



$U_e \approx 0$  if the output goes to the inverting input  $\Rightarrow$  negative feedback

$$U_{in} - U_{out} - U_e = 0$$

$$U_{out} = U_{in}$$

$$I_+ \approx 0 \Rightarrow Z_{in} = \frac{U_{in}}{I_+} \approx \infty$$


Impedance

Transformer

Impedance :

= Resistance

4.) Non Inverter

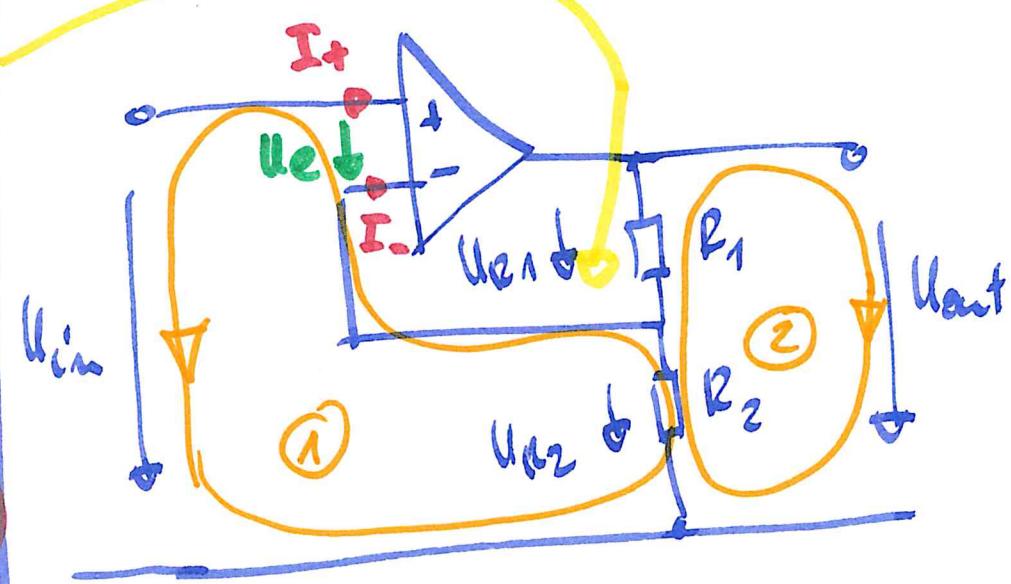

④

$$I_+ \approx 0; I_- \approx 0 \quad ⑬$$

⑭

$R_2 \parallel R_2 \quad U_{in} - U_{R2} - U_e = 0$

$\downarrow$   
 $\approx 0$

$(U_{in} = U_{R2})$

$U_{out} - U_{R2} - U_{R1} \quad U_{out} \sim$

$(U_{out} - U_{R2} - U_{R1} = 0)$

$U_{out} - U_{in} - U_{R1} = 0$

$\checkmark \frac{R_1}{R_1 + R_2} \cdot U_{out}$

$U_{out} \left( 1 - \frac{R_1}{R_1 + R_2} \right) = U_{in}$

$$U_{out} = \frac{1}{1 - \frac{R_1}{R_1 + R_2}} \cdot U_{in}$$

$$= \frac{R_1 + R_2}{R_1 + R_2 - R_1} \cdot U_{in}$$

$$= \frac{R_1 + R_2}{R_2} \cdot U_{in}$$

$$U_{out} = \left( 1 + \frac{R_1}{R_2} \right) U_{in}$$

Non Inverter