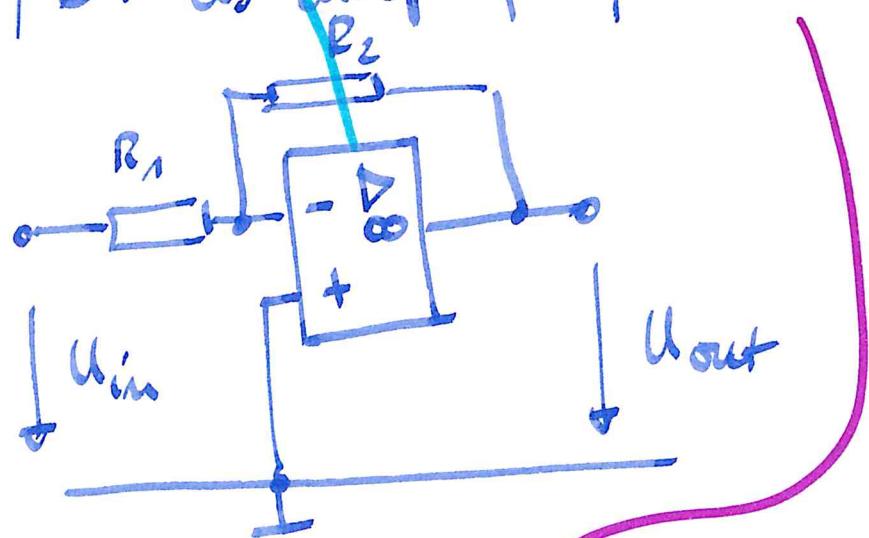


# Electronic devices, 16.06.19

①

## Summary OP


1.) OP as amplifier, inverted



$$\text{voltage gain } \approx = \frac{U_{\text{out}}}{U_{\text{in}}} = - \frac{R_2}{R_1}$$


$\left. \begin{array}{c} \Delta \\ \infty \end{array} \right\}$  ideal OP

2.) OP as amplifier, not inverted

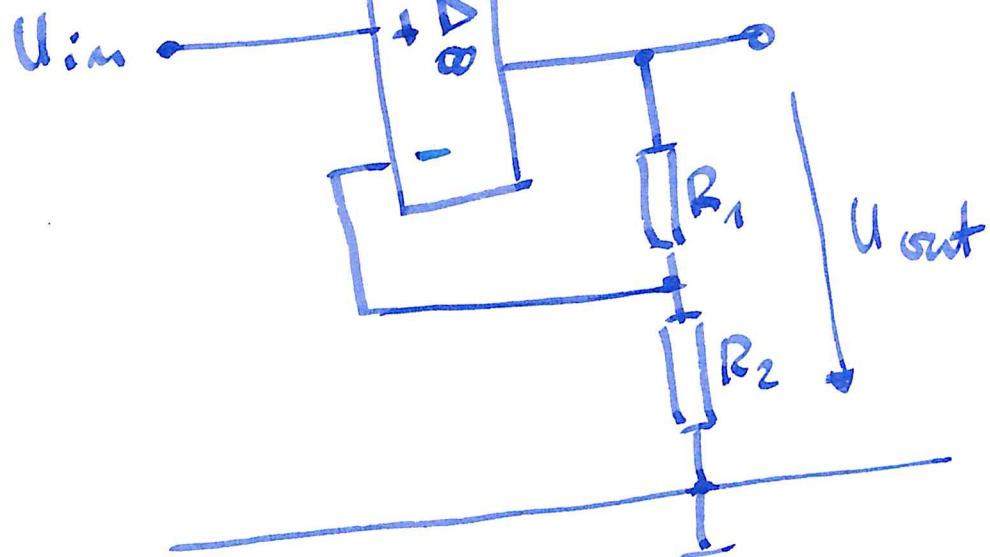

$$\text{voltage gain } \approx = 1 + \frac{R_1}{R_2}$$

3.) OP as impedance trans-former

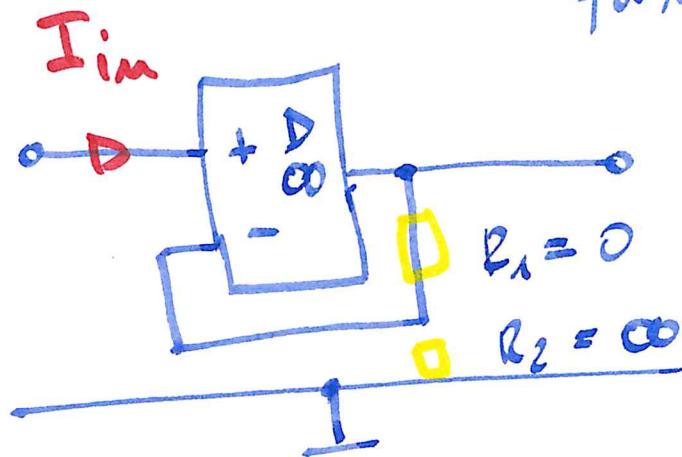


$$v = 1 + \frac{R_1}{R_2} = 1 + \frac{0}{\infty} = 1$$

$$I_{in} \approx 0$$


$$Z_{in} = \frac{U_{in}}{I_{in}} \rightarrow \infty$$

Input impedance

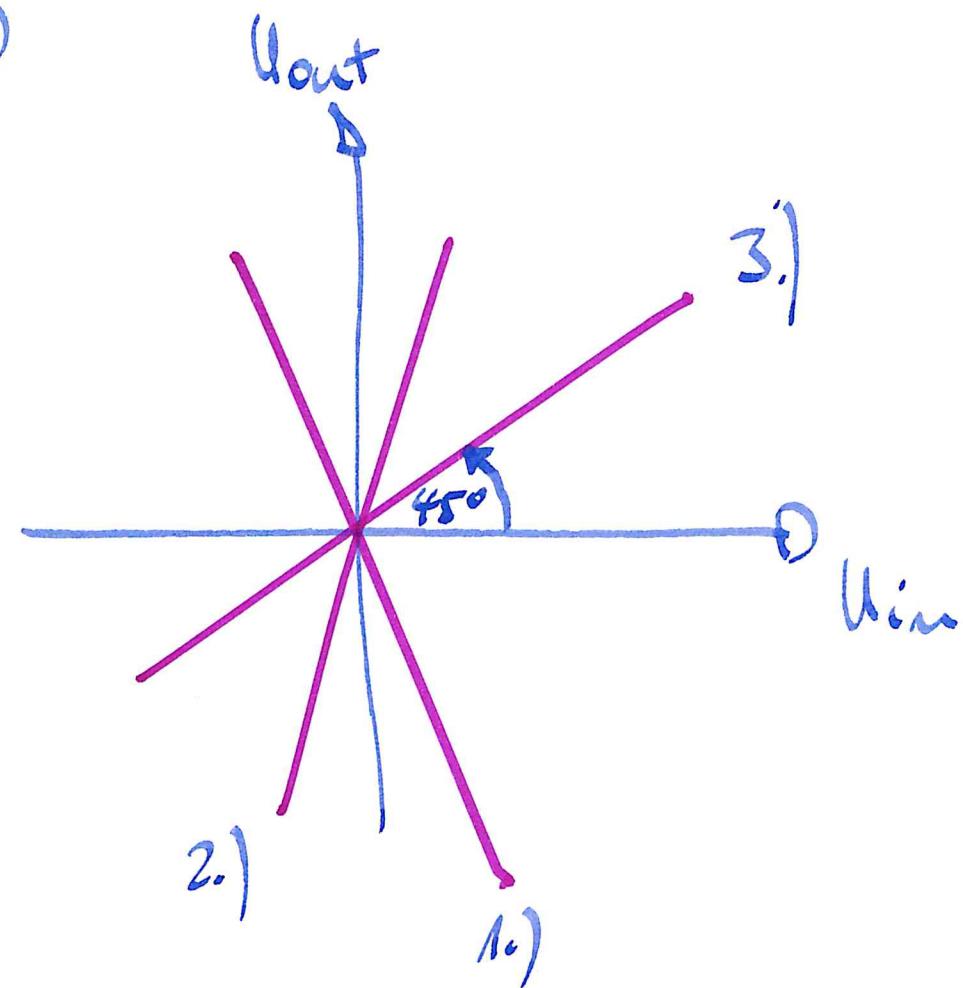

$$\left. \begin{array}{l} v = 1 = \frac{U_{out}}{U_{in}} \\ \Rightarrow U_{out} = U_{in} \end{array} \right\}$$

## f.) Filtering

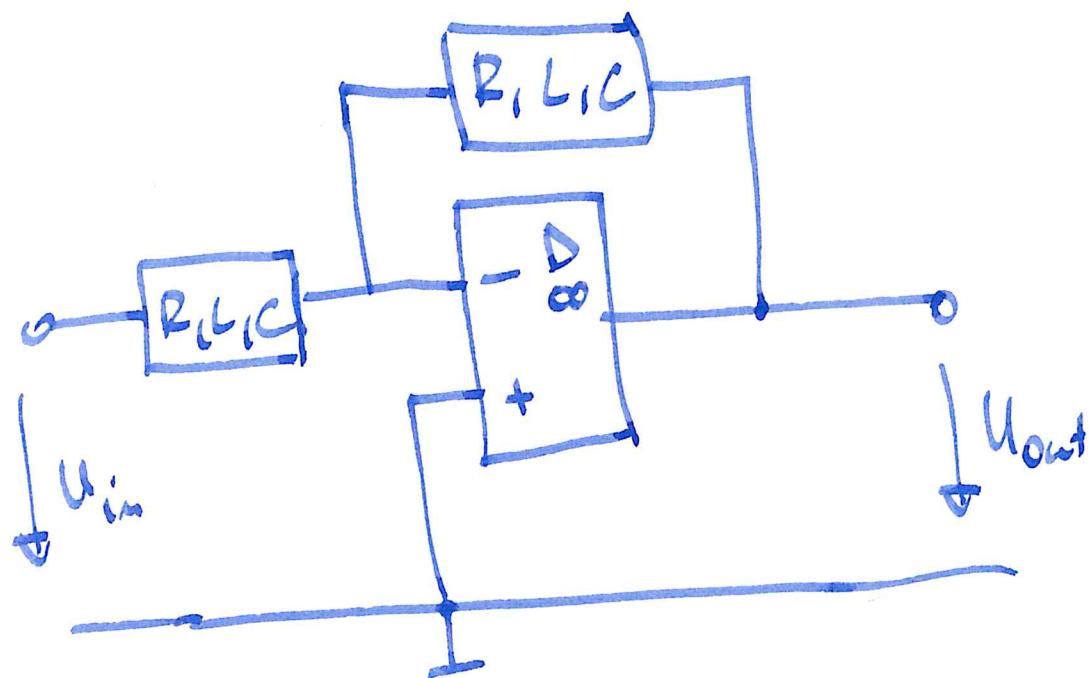


$\boxed{R, L, C} \hat{=} R, L, C - \text{Net Work}$

→ see Wikipedia Butterworth Filter

⑤


⑥

Filter 1

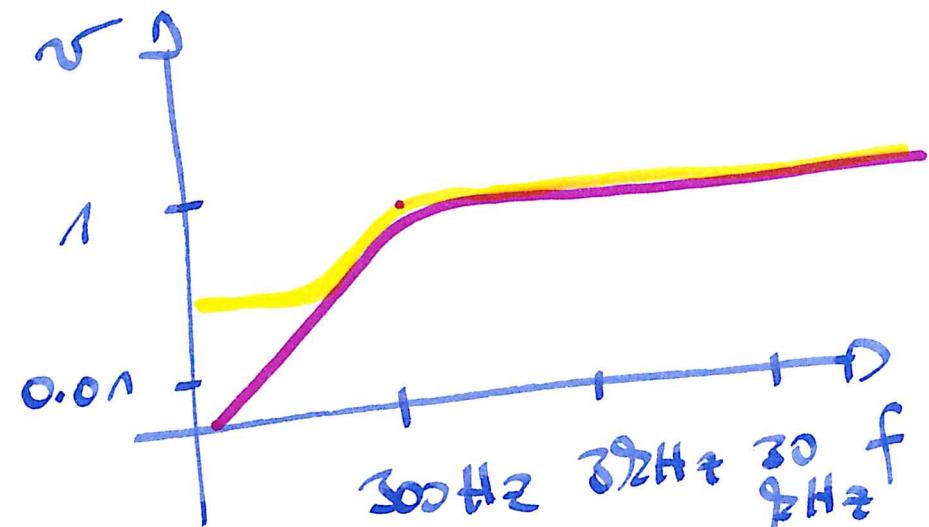


⇒ The gain depends on the frequency

Filter 2:

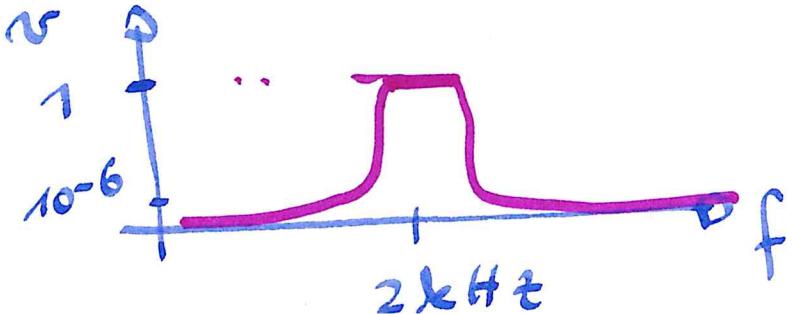

## Filter 3: Power LAN

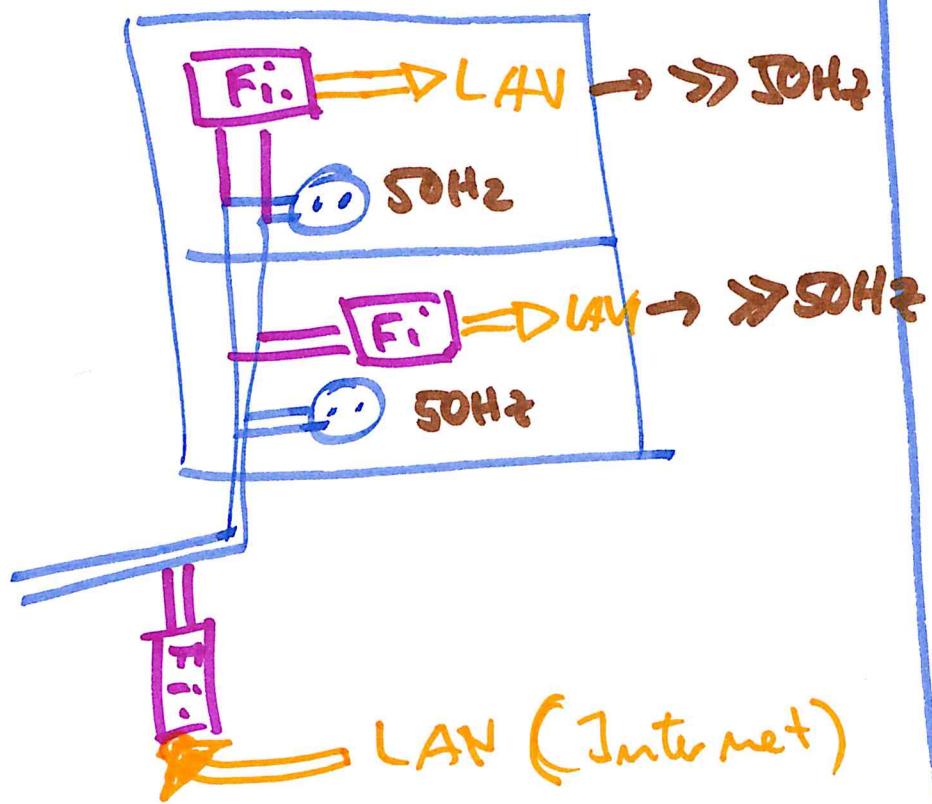

(E)


(R)

## 5.) Applications of OP

in ADC, DAC

} All our receipt  
yesterday - , Friday

## 6.) More :

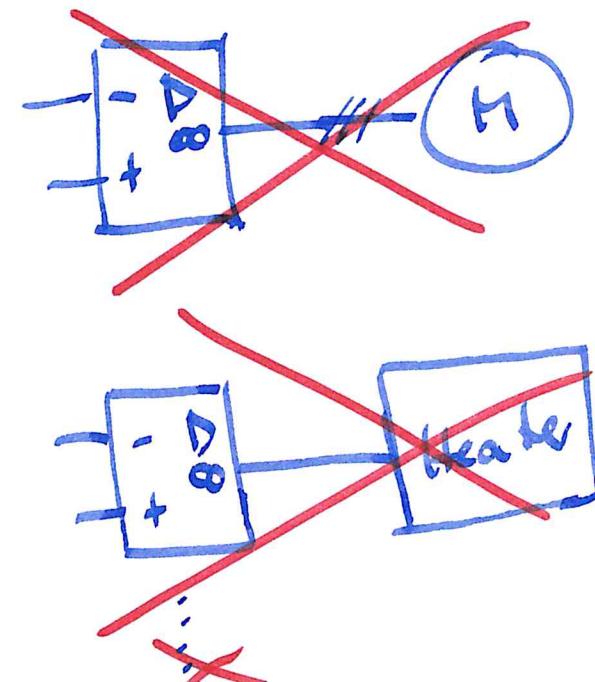


$\Rightarrow$  it is not possible, ⑨ because the output power is too small.

$\Rightarrow$  therefore we use

- relais, contactors
- transistors, thyristors
- diodes

relais,  
contactor

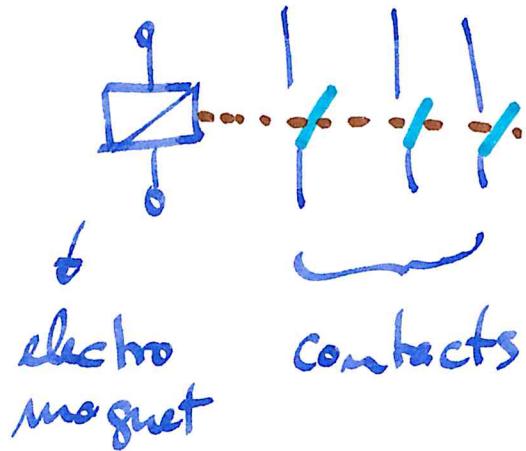


$\Rightarrow$  here page 5 of script ET15  
TT


⑩  $\Rightarrow$  here page 6 of script ET15  
TT

## 7) Diodes in application


- One way rectifier

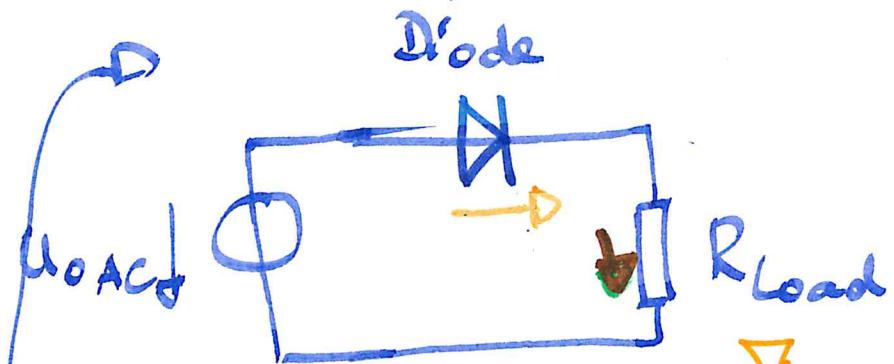

Diode :


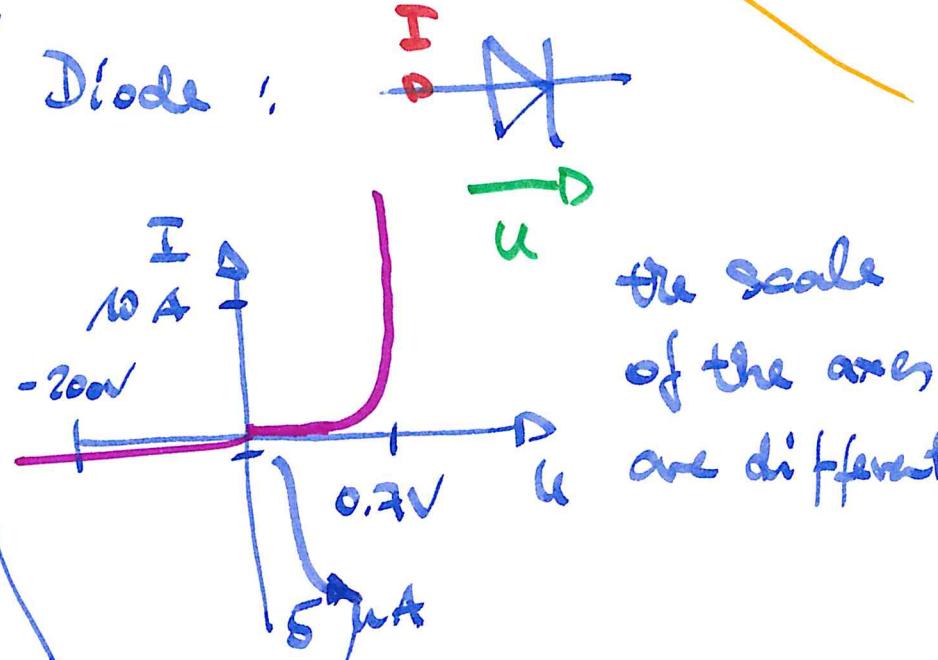


(if the scale is not different ⑪)

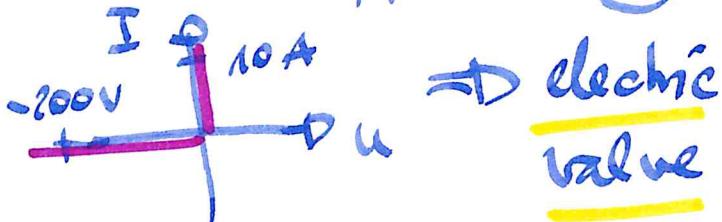


⑫ (also called half wave rectifier)

- full wave rectifier, bridge rect.

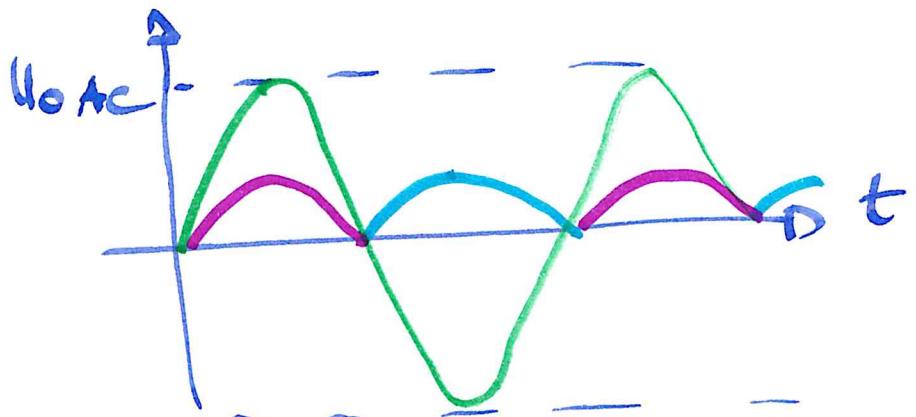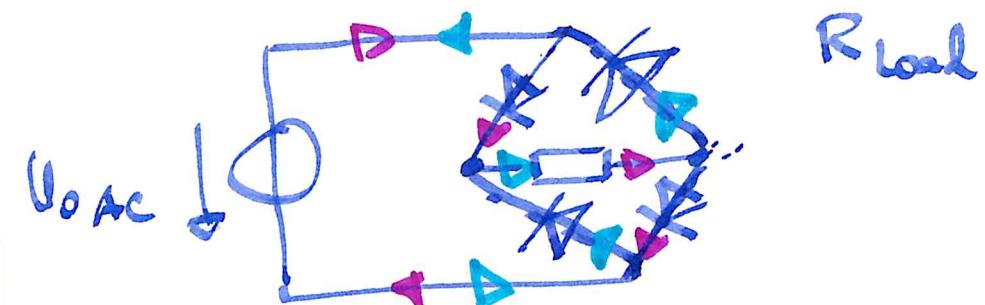


example for valve:

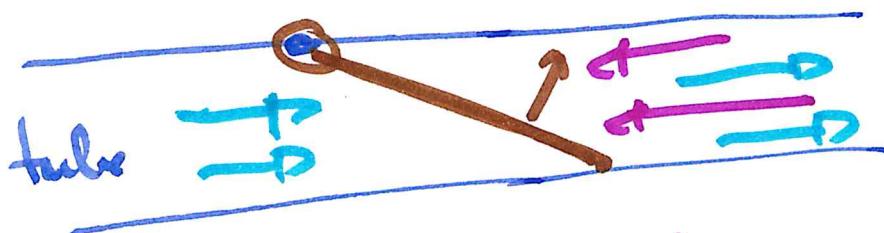

water  
can go


water  
can not go

Molar:

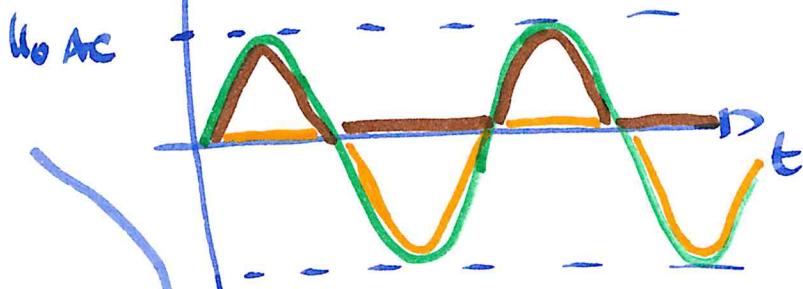


better circuit diagram

AC 1 phase

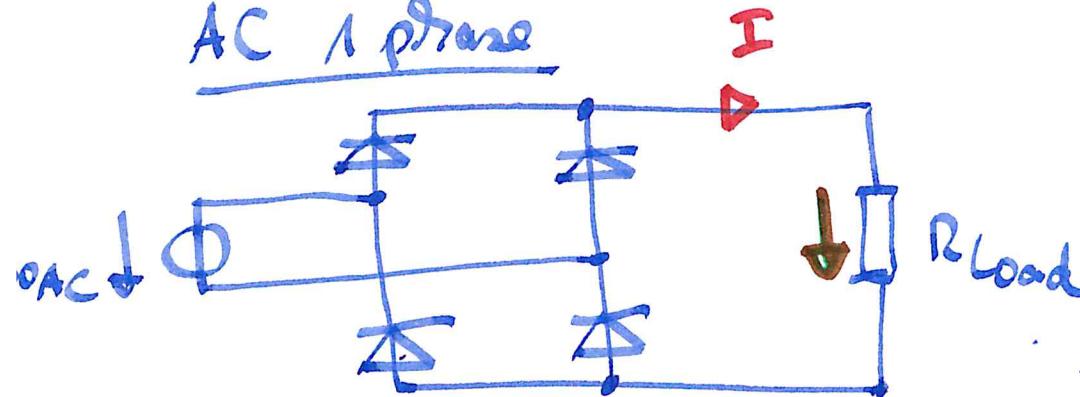

(13)

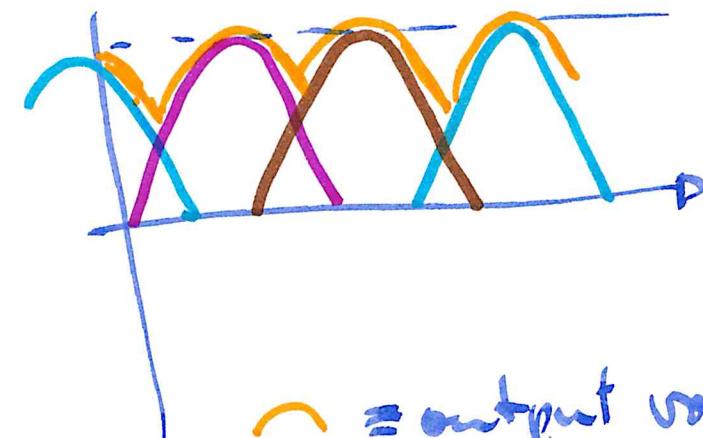(14) or. 3 phase bridge rectifier  
bei google




~ = output voltage:

moderat


smallest voltage  
tipple ? + ++

AC 3 phase

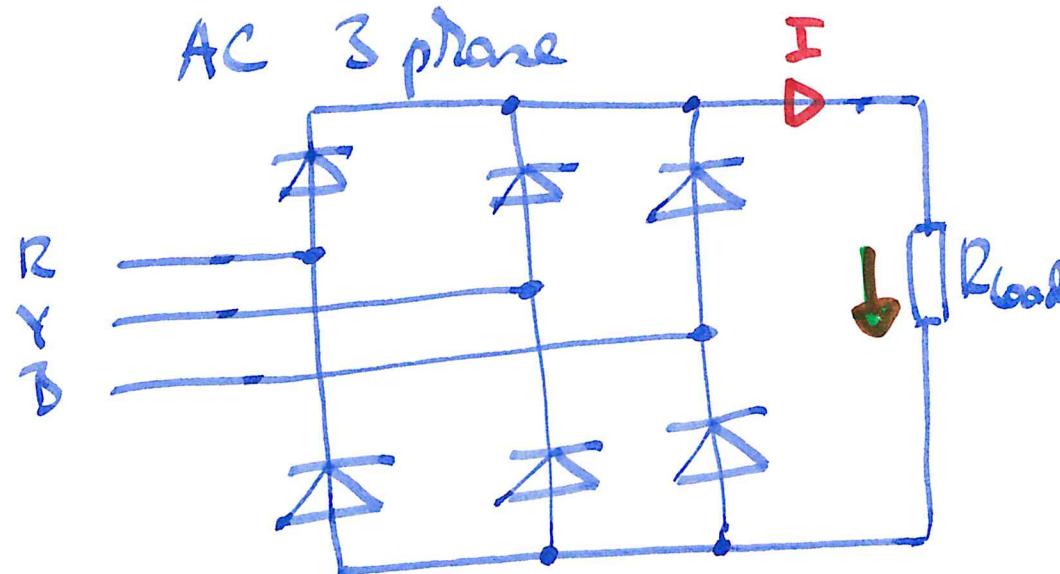


voltage dia gram see: Wikipedia:  
Dreiphasengleidrichter

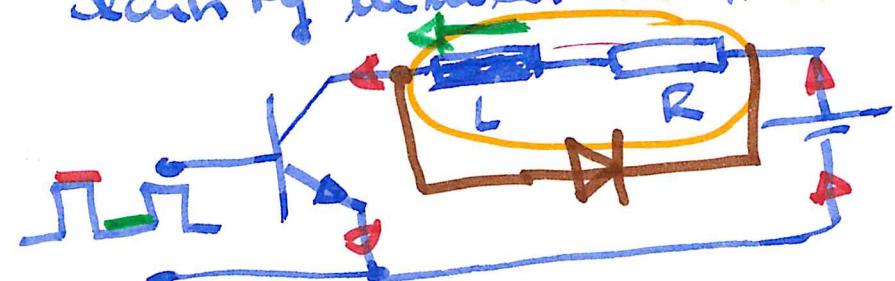Another application of a diode:  
Security element in switching




⑮

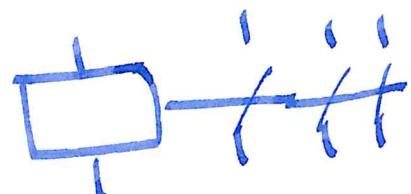

:

Can  
be  
repre-  
sented

⑯

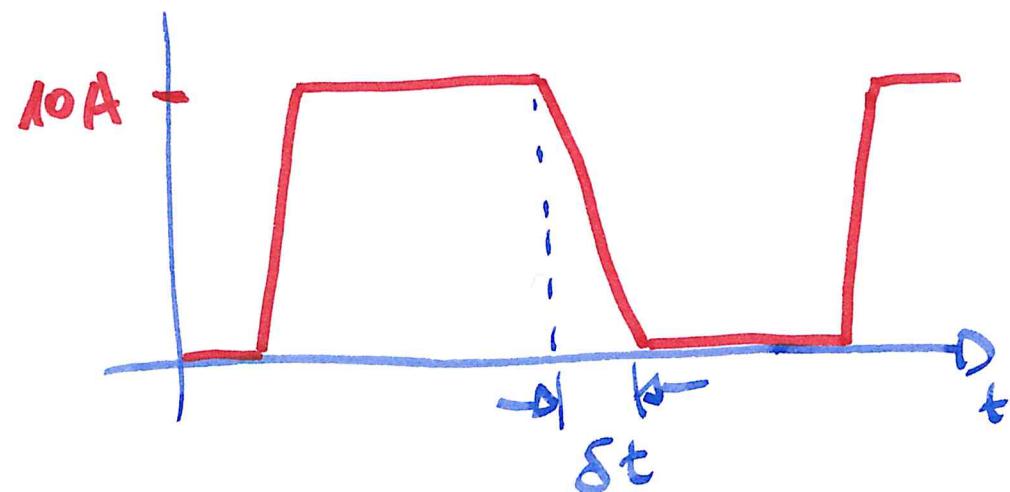

this  $\delta t$  is very small,  
for ex. 1ms, 10μs ...

photo

⑯


$$I, i \leftarrow u_L$$

~~current~~

~~current~~

~~current~~

$$u_L = L \frac{di}{dt}$$

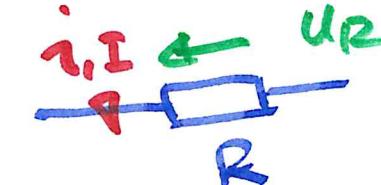

$$u_R = I \cdot R$$

example

$$L = 2H ; \delta t = 10\mu s \quad 10ms$$

$$\Delta I = \delta I = 0A - 10A = -10A$$

$$u_L = 2H \cdot \frac{di}{dt} = 2H \frac{\delta I}{\delta t}$$

$$= 2 \frac{V}{A} \frac{-10A}{10\mu s} = -20 \frac{V}{10\mu m}$$

$$= -2 \cdot 10^6 V = -2MV - 2kV$$

$\Rightarrow$  Diode same side