


① ②

Repeat:


- Diodes
- Z-Diodes
- Photo Diodes

- Photo diode can be a general Si-diode, can be from other material

Sensitivity of photo diodes:

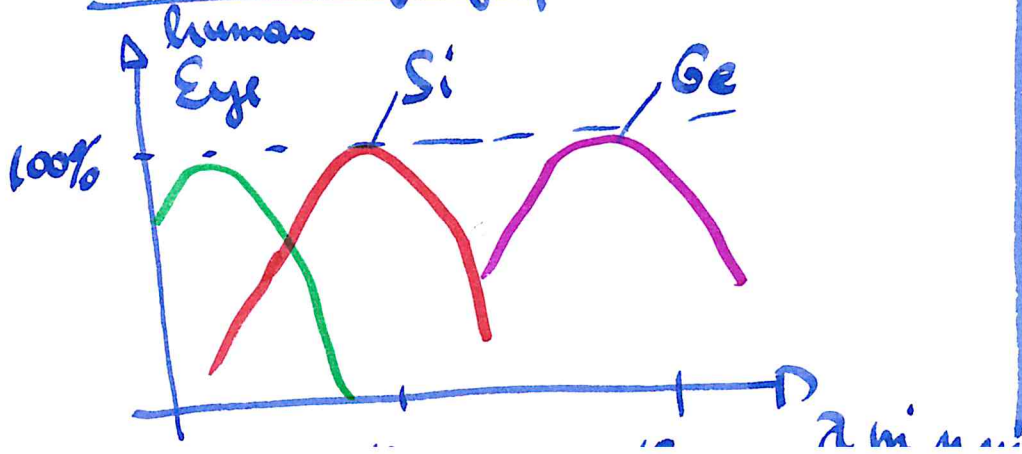

Characteristic of a diode

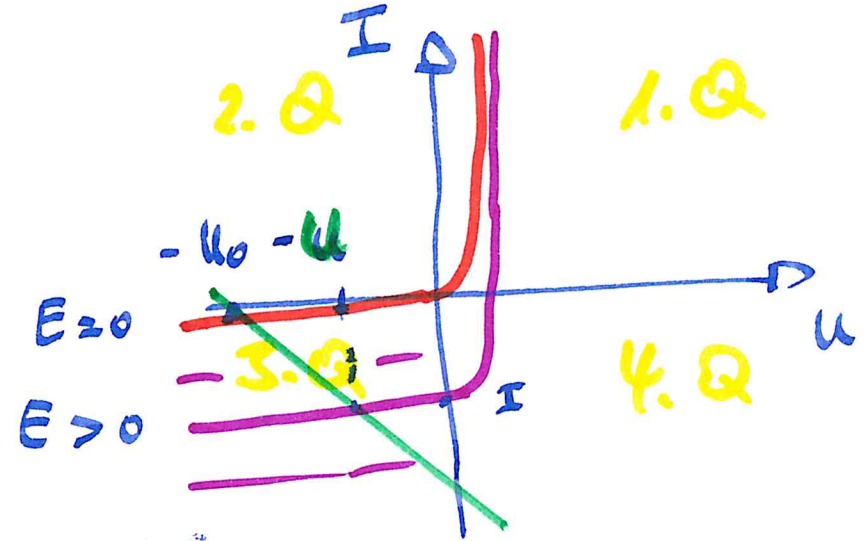

$E$ : ~~light~~ radiation


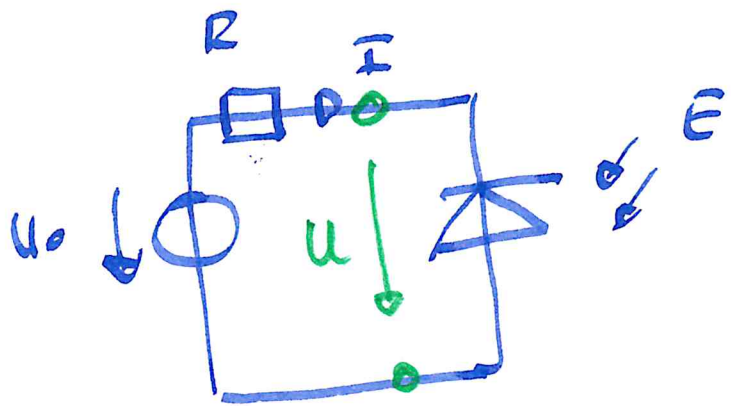


Photo diode works in reverse direction

# Photo diode characteristics


Curves:

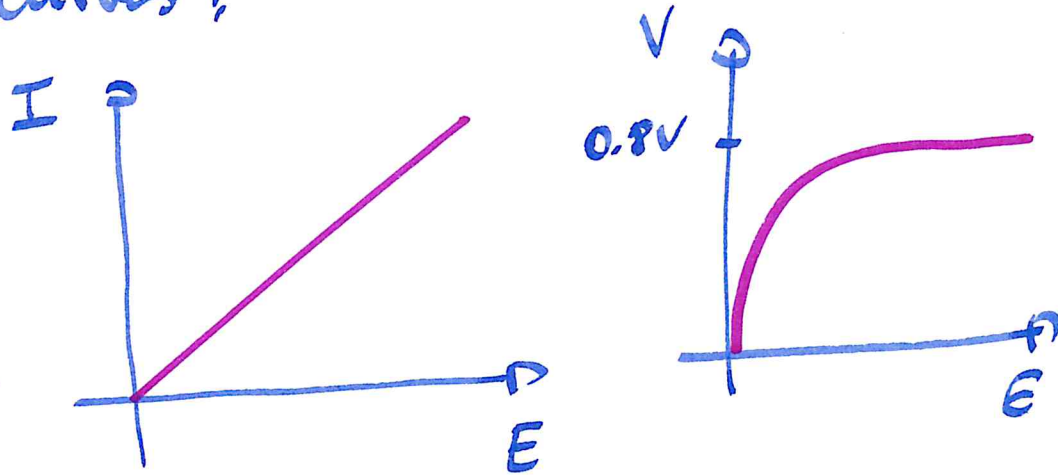
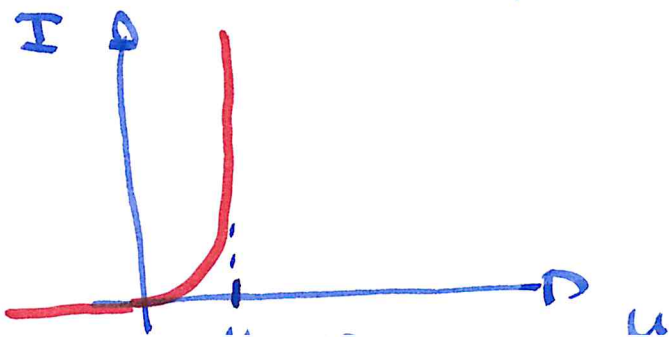
## • LED

= inverse photo diode

- you can get in diff colours
- LED works in forward direction




③


④

$U_{LED}$  depends of the colour of the LED, 1V, 2V, 3V

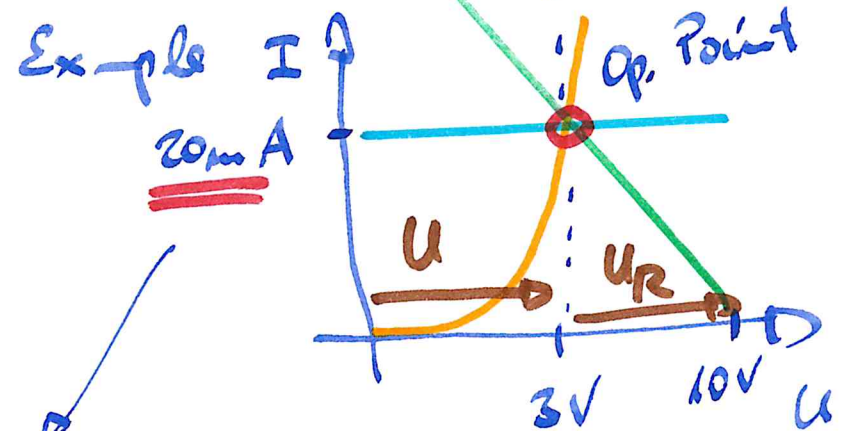LED's are not controlled by the voltage, they are more controlled by the current.



$$I_{LED} \leq 20 \text{ mA}$$

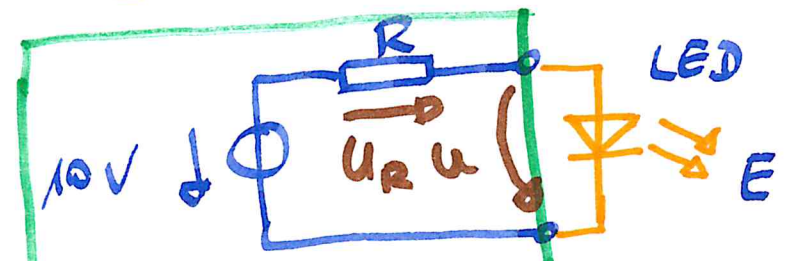


$$U_R + U = 10V; \quad U_R = 10V - U = 7V \quad (5)$$

with  $I = 20mA \Rightarrow R = \frac{7V}{20mA} = \underline{\underline{350\Omega}}$


Sun's

PV-Cells

- Theory as in Lucas Nülle

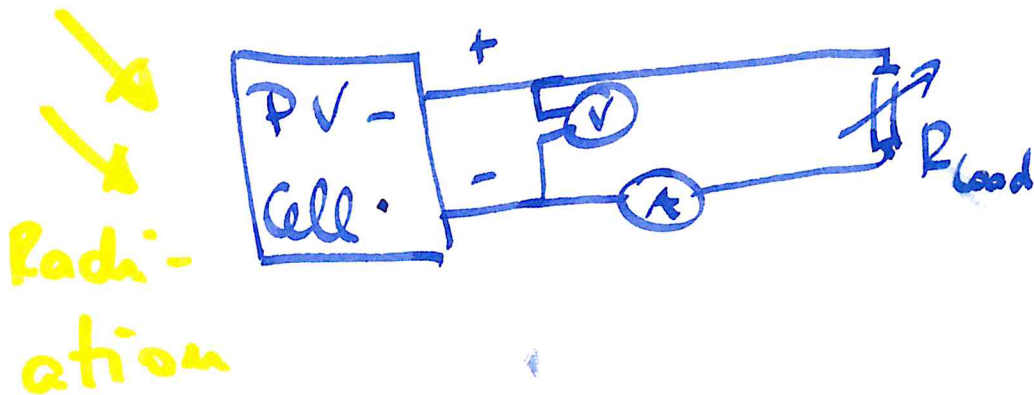

(6)

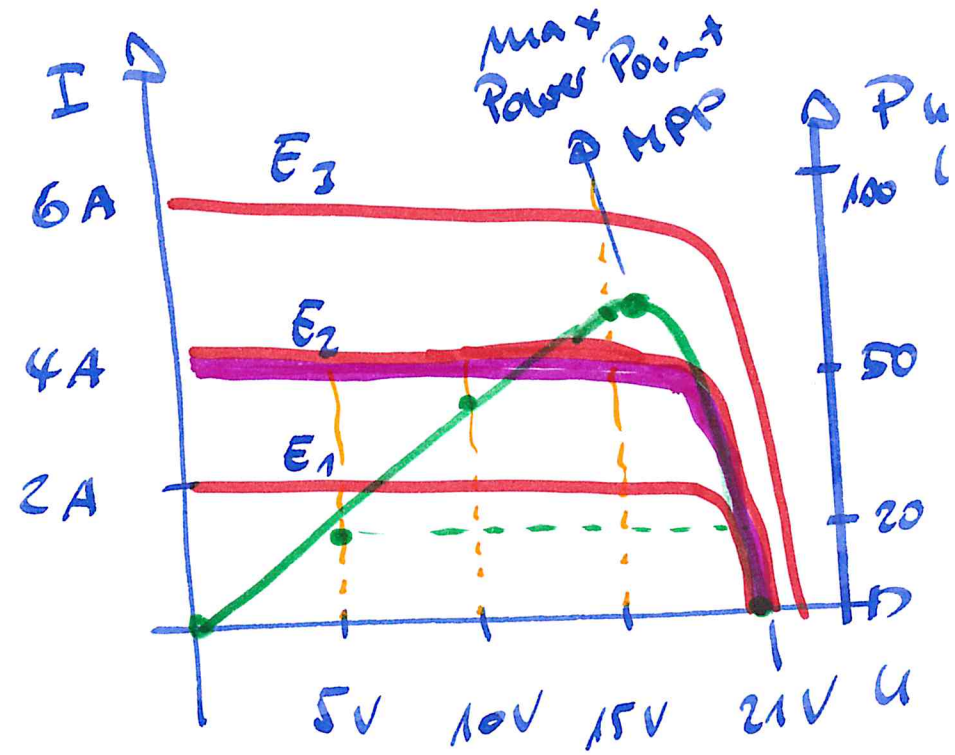

$$P = U \cdot I$$

Only in MPP the PV-Cell produces the max ~~to~~ power.  
MPP is not always on the same point, see